computing today No 2

December 78

Win a Triton

THE NEW MAGAZINE FOR SMALL SYSTEMS WITH BIG IDEAS



Presented as a supplement to ETI.

Hop on a Nasbus to 32K of memory now

The Nascom — 1 is designed with expansion in mind. This is made possible by using the best products available. The Z80 microprocessor incorporated in the basic system is so powerful it can support 64K bytes of memory and 256 ports. To utilize this capability, we have designed the buffered 77 — way Nasbus.

With this arrangement, the way is clear for considerable expansion, starting with our new memory expansion board. It has 16 memory sockets and two EPROM sockets. Therefore, you can fill it with 4K dynamic RAM up to a maximum 8K or with 16K dynamic RAM up to a maximum of 32K. A 2K Tiny BASIC in EPROM has been developed for the board.

To go with the board, we have produced a very flexible I.O board with three PIOs each giving two, 8bit ports, plus a UART for serial interface.


As you start building up your Nascom system you will need a convenient means of storing boards. Our new, custom-designed, Vero frame

will allow for a Nascom -1 to link through a buffer board to a 77-way Motherboard. There is then the option of eight or more expansion boards. To power this capability there is a new 8.5 amp power supply especially designed for the frame.

No other system offers so much at such a low cost. And it all starts with the basic Nascom — 1 kit which for just £197.50 offers an intelligently usable system with video and cassette interface, a full alpha-numeric keyboard and a mighty CPU chip. So if you want the best — make it a Nascom system.

Nascom-1 Kit still only £197.50 +VAT



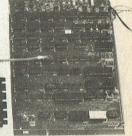

Nascom Expansion — Prices

Buffer Board Kit	£25.00
4K RAM Board	£70.00
16K RAM Board	£179.00
4K RAM (4027)	£35.00
16K RAM (4116)	£106.00
Tiny BASIC	£25.00
2.2amp Power Supply	£24.50
Prices exclude VAT	



92 Broad Street, Chesham, Bucks. Tel: (02405) 75151

UK National Distributors

Barrow-in-Furness
Camera Centre

Tel: 0229-20473

Torquay

CC Electronics

Tel: 0803-22699

Egham & Manchester

Electrovalue

Tel: 07843-3603

Glenfield, Leicester

Eley Electronics

Tel: 0533-8771522

London W2

Henrys Radio

Tel: 01-723 1008

Oldham, Lancs Lock Distribution

Tel: 061-652 0431

Chesham, Bucks
Lynx Electronics

Tel: 02405-75151

Liverpool L2
Microdigital

Tel: 051-2360 0707

New Barnet, Herts

Comp Components

Tel: 01-441 2922

Airamco Ltd. MICRO COMPUTER PRODUCTS

Distributors for JADE COMPUTER PRODUCTS
All products brand new with full industrial specification

BARE

S100 COMPUTER CARDS KIT	ASSEMBLED	BOARD
Mother Board £71.00 Desk Top Rack, 12 slot mother	£82.50	£26.25
board + 15A @8V, 2A @ ± 16V	To the second	
15A @8V, 2A @ ± 16V		Control Section
Jade 8080A CPU BOARD £75.00	£122.50	£22.50
Jade Z80 CPU BOARD 2MHz .		As Salar
£99.95	£138.75	£26.25
Jade Z80 CPU BOARD 4MHz	£149.95	€26.25
Jade Serial / Parallel I / O BOARD	£149.95	220.20
£93.70	£134.29	£22.50
Jade 2708/2716 EPROM		Mary Name
BOARD £44.95	€82.46	£22.50
(16x2708 or 2716) WITH 8	6104.00	622.50
2708s £97.46	€134.96	£22.50
Jade REAL TIME CLOCK BOARD £93.71	€134.96	€22.50
Problem Solvers 16K STATIC	3.000	
RAM 450nS ——	£270.00	6 8 8 6 1 - 1 - 1 - 1 - 1 - 1 - 1 - 1 - 1 - 1
16K STATIC RAM 250nS	£296.00	Ge
Jade 8K static RAM BOARD		
450nS £94.50 Jade 8K static RAM BOARD	£112.50	€19.95
350nS £104.95	£119.96	€19.95
Jade 8K static RAM BOARD	£119.96	£19.95
250nS £127.50	£142.50	€19.95
S.D. Sales "EXPANDORAM"		
Dynamic Memory 375nS access		Salar Salar Barre
time 8K £113.25 Memory 375nS access time 16K		Sala De la constitución de la co
Memory 375n5 access time 16k	£229.00	£189.00
Memory 375nS access time 32K		
£297.00	£337.00	£297.00
Memory 375nS access time 64K	05	0510.00
£513.00	£553.00	£513.00
VERSAFLOPPY DISK CONTROL- LER (up to 4 drives 51/4 or 8)		
C11 7E	£165.00	and the second
SHUGART 8 Drive	£385.00	No.
SHUGART 8 Drive PERTEC 51/4 Drive	£225.00	- A-12
CONC. III CONTROL OF THE PROPERTY OF THE PROPE	AND REAL PROPERTY AND ADDRESS OF THE PARTY AND	£1.20
Components 2708 1024x8 EPROM £6.99	21L02-1 450nS	67.92
2716 2048x8 EPROM £29.90	21L02 250nS	£1.40
(intel)	8 for	£9.60
2516 2048 x 8 EPROM	2112-1 256x4 (45	O) £2.25
£29.90	4044 4Kx1 (450) 4045 1Kx4 (450)	£7.45
(equivalent of above) T.I. 1702 256x8 EPROM £4.85	New Device MK41	18 N4 (24
2104 4096x1 DRAM £3.50	pin) 1k x 8 bit stati	
8 for £26.00	NS. Similar pin o	ut to 2708
2107B-4 4096x1 DRAM	EPROM. Price £1	6.50. Each
£3.50	data available.	62.40
8 for £26.00	8212 8216	
Note New Low Prices 16K	8224-4	£7.46
4115 5kM DRAM £9.99	8226	£2.95
4116 16kx1 DRAM £14.99	3881	£9.50
8 for £108.00	3882	
6821P PIA £5.90	S100 Skts	£3.30
AY 51013 UART £4.50	Textool 24 pin Zero	65.60
AY51014 UART(5V) . £6.50 AY53600 ENCODER . £9.99	force Skt 4115 8kx1 DRAM 81LS95	£9 99
8080A CPU £8.99	81LS95	£1.25
00007 01 0	81LS97	£1.25

All Prices EXCLUDE VAT @ 8%.

Trade discounts on Quantity Please add £1.00 P&P for \$100 items then add VAT @8%.

24-hr. Ansaphone order service with ACCESS or BARCLAY-CARD. MAIL ORDER ONLY





For components please add 40p P&P, then add VAT @ 8%.

AIRAMCO LTD.
30 WITCHES LINN
ARDROSSAN
AYRSHIRE
KA22 8BR
TEL. 0294 65530
TELEX 779808 RAMCO

Semiconductor prices are always changing and the trend is generally downwards. So ring for latest up-to-date details.

computing today

No.2 December 1978

News	4	News for MPUs
PTAs Explained	6	The INS and OUTS
BASIC Explained	10	Speaking basically
Book service	15	Book Bargains
Microbiography	17	8080 under the Microscope
TRITON Competition	20	Cross-number Puzzle
EPROM Programmer	23	Blow your own
Softspot	31	Software Section

EDITORIAL ADVERTISING PRODUCTION

Halvor W. Moorshead
Ron Harris B.Sc
Gary Evans
Jim Perry
Phil Cohen B.Sc
John Koblanski
Steve Ramsahadeo
Paul Edwards
Margaret Hewitt
Andrew Scott
Kim Hamlin, Bren Goodwin
Tim Salmon, Val Tregidgo
Mark Strathern (Manager), Tom Moloney
Joy Cheshire, David Sinfield

INTRODUCTION

We do not plan a regular editorial page in Computing Today for the simple matter that we'd soon run out of things to say — try looking at the editorial pages of other magazines for ample evidence of this.

This month, however, we'd like to take this opportunity of making the familiar plea of all new magazines — please let us know what you think of us we've had a couple of interesting comments on last month's issue but we would like to think we have slightly more than ten readers with something to say if you happen to have the odd article describing some aspect of personal computing we'd also be glad to hear from you.

Last month we omitted to credit the authors of a number of items to put the record straight Howard Birkett was responsible for the NASCOM 1 review, Phil Cornes for part 1 of the BASIC explained series and Don Scales for the item on the Triton's BASIC.

Errors noted in the Triton article are: 1) On page 31 of November's ETI the keyboard connection diagram should have shown the third output down on the right-hand side of the diagram as not strobe. 2) Strictly speaking the reset signal at the extender socket is not buffered and should have been marked as such.

MICRO-COMPUTER BARGAINS

We have a stock of untested microcomputer PCB's which are surplus to our requirement. Each board contains an Intel 4040 (CPU), 4201 (Clock), 4289 (Standard Memory Interface), 5MHz crystal, zero crossover detector cct, power on reset cct, skts for 6 x 1702A PROM and on board power supply containing transformer, rectifier, regulator, heatsink and reservoir capacitor.

These PCB's are sold with data on all chips and cct diagram, as untested units at the bargain price of

£19.00 ea

Also available:

1702A memory, used but erased

£6.00

1702A memory programmed to your requirement £7.50
6265 gen purpose i/p-o/p device
£5.00

Cheque / Postal Order to:

VERDURE LTD.

54/64 Morfa Road Strand, Swansea

Mail Order Supplies Only

Tel: (0729) 41241/462684

HAPPY MEMORIES



ASCII KEYBOARDS £49

£1 p&p. Cursor Kit £2.50

All 128 ASCII characters, parallel output, 2 key rollover, Alpha lock, Auto-repeat, Two user-definable keys, positive and neg. strobe, All on 12½ x 6 inch PCB. Add-on five key cursor kit for up, down, left, right and home available. Send SAE for data sheet.

Science of Cambridge Mk 14. £2.80 Set of 18 Texas low-profile DlL sockets. 2ILOs 450ns 95p, 16 up 92p, 64 up 89p 2ILO2 250 ns 110p, 16 up 107p, 64 up 104p 2114 300 ns 625p, 4 up 600p 4116 DRAM 1250p 4 up 1200p 2708 450 ns 725p, 4 up 700p

Texas low-profile DIL sockets:
Pins 8 14 16 18 20 22 24 28 40
Pence 10 11 12 17 18 20 22 28 38
Antex 1mm bits for CX17 or CCN irons **45p**

Happy Memories, 5 Cranbury Terrace Southampton, Hants SO2 0LH

All prices include VAT. Add 20p postage except where shown. COD available at cost.

AT LOW COST

Texas Talk

We've been hearing stories about Texas's entry to the hobby/education/business computer markets for some time. Like so many other Texas product launches before it, the stories around for months before the first sight of any hardware, lead to a sense of anti-climax at the official unveiling.

Hopes that the machines will not be waiting in the wings for too much longer, however, are strengthened by the fact that Texas's European Consumer Division have just appointed a personal computer manager. The machine should be worth the wait for it is Texas's view that a late entry into a competitive field, such as home computing, means that the product must enter on a technological cusp. What will they offer us for our money. Views vary but most seem to suggest that the Texas machine will include some form of fast access, fast transfer, form of mass storage - (floppy?, Bubble??), We say the machine is expected soon it must be - though we were disappointed when we heard the latest pronouncement on the reason for the delay — Texas did not want to get caught up on the Christmas novelty market and so had decided to launch next year.



The research machines 380Z system has been with us for some time now Z80 based, the system in its basic form consists of a by now familiar configuration — the 380Z itself with a standard domestic TV or video monitor to provide output and a cassette recorder for back up storage.

The recent addition of a mini-floppy system to the 380Z's hardware will greatly increase the scope of the system. The mini-floppy is offered with one or two drive's each with a 70K capacity BASF drives are used and the price includes Digital Research's CP/M disc operating system, rapidly becoming the industry standard for Microcomputers.

Research Machines will be able to offer several BASIC interpreters and compilers — FORTRAN and

News

COBOL will rollow. In addition, purchase of the system from Research Machines will secure membership of the CP/M user's club with access at nominal cost, to the user's club library, already running at 14 volumes.

Singleboard Superboard

Due in this country before the end of this year, the Ohio Scientific Inc Superboard 2, is a machine to look out for. The system is built on a single board — even the keyboard is on the PCB — all that is required is a 5V 3A PSU.

Based on the 6502 MPU, PET, APPLE et al, with an 8K BASIC and up to 8K of static RAM, the Superboard 2 packs quite a processing punch.

The onboard keyboard is a 53 key design providing upper and lower case plus some user programmable functions. Also included is a Kansas City tape interface.

The output is to a video monitor and the display is a 24x24 format that provides graphics as well as alpha-numeric characters.

Available options include an expander board that features 24K of static RAM, a dual mini-floppy interface and a port adapter for printer and MODEM.

The machine — can you wait? — should be available here at a cost of £284.95 — what do you say about that Commodore?

People Like Petsoft

Petsoft have arranged a reciprocal deal with Personal Software Inc, a large American Microsoftware house, with the result that PETSOFT'S large range of software will now be distributed in the States and Canada and some of Personal Software's best titles will be available from PETSOFT.

The Microchess program (£14) is one example of Personal Software's work and at the low asking price, should be well received over here.

The PETSOFT catalogue is running at about 100 titles covering everything from games to business packages and software tools. An SAE to PETSOFT at the address below will secure their catalogue. PETSOFT, P.O. BOX 9, NEWBURY, BERKSHIRE, RG13 1PB.

4

The exciting new

Personal Computer exclusively from:



Building a better computer wasn't easy—but we did it.

Complete kit of parts available only £286 (+ VAT)

Basic in Rom: a powerful 2k Tiny basic resident on board, makes Triton unique, easy to use and versatile.

Grahics: 64 Graphic characters as well as full alpha numerics.

Single Board: Holds up to 8k of memory, 4k RAM and 4k ROM, supplied with 3k ROM and 2k RAM.

Memory Mapping: 2 mode VDU, 1/0 or memory mapped for animated graphics.

Cassette Interface: crystal controlled Modem tape I/O with auto start/stop + ''named'' file search.

UHF TV Interface: On board uhf modulator, plugs into TV aerial.

Comes Complete with KEYBOARD, CASE, POWER SUPPLY, THRO-HOLE PLATED QUALITY P.C.B. FULL DOCUMENTATION POWERFUL 1k MONITOR & 2k TINY BASIC PLUS ALL COMPONENTS INCL. IC SOCKETS. NOTE TV SET & CASSETTE NOT IN-CLUDED.

Expansion: Fully buffered for up to 65k of memory on expansion busbar.

To TRANSAM COMPONENTS LTD. I am interested in the Triton 12 CHAPEL STREET, NW1 Please send me the following Name_ A copy of your latest catalogue I enclose 30p + S.A.E. 9 × 7 Address (please print) A copy of the Triton Manual l enclose £5 + 30p P & P A complete kit of parts for Triton Computer, £286 + VAT + £4 P & P

A Printed Circuit Board £50 + VAT & £1 P & P ETI 9

TOTAL ENCLOSED £


Cheque, Money Order, etc

All components can be bought separately and eleven packs can be purchased on an easy-to-buy scheme. See catalogue.

The P.C.B. alone is £50 + VAT plus £1 for packing and postage.

TRANSAM COMPONENTS LTD. **12 CHAPEL STREET** LONDON, NW1 TEL: 402 8137

 NEXT TO EDGWARE ROAD TUBE STATION, MET. LINE TRITON COMPUTER IS THE TRADE MAKE OF TRANSAM COMPONENTS LTD.



ORDER

BARCLAYCARD, ACCESS, VISA & MASTER CHARGE ARE WELCOME. SEND

YOUR CARD NUMBER WITH

PIAs Simplified

Ron Wilson explains the operation of a typical PIA (Peripheral Interface Adapter), clearing up the confusion often caused when a data sheet is consulted by a novice to the art of I/O. A 6800 based system is taken as an example for this article.

ON THE PIA THERE are 16 bi-directional lines that can individually be made to act as straightforward inputs or outputs. The 8 bit structure of the 6800 dictates that these lines are separated into an A group and a B group each of 8 bits. The internal register structure of the PIA is shown from the users viewpoint in Fig. 1. The A register group and the B register group each consist of a Control Register, Data Direction Register, and Data Register. It is to the data registers that the two sets of bi-directional data lines are connected. The 6800 system is organised so that the microprocessor treats the PIA registers as memory locations. The PIA can be addressed and will respond to instructions in the same way as memory.

The documentation that arrives with the readybuilt microcomputer board obtained by the user will specify the PIA addresses for that system. A particular PIA might be located, for example, at addresses 8004 to 8007 inclusive. (The number system used is

normally hexadecimal).

In this case the A side registers have been allocated


8004 and 8005 whereas the B side registers occupy locations 8006 and 8007. Each side has thus two addresses available to access three registers. How can three registers be accessed with only two addresses?

The address 8004 is given to two registers, the 'A' Data Direction Register and the 'A' Data Register. The required register is selected, from these two, by programming bit-two (b2) in the Control Register. The Control Register is at location 8005. When b2 is logic 0 the Data Direction Register is selected. Conversely when b2 is logic 1 the Data Register is selected. The user's aim is to configure output and input lines, so particular cases will now be illustrated.

The cases described have each been tested and work correctly. It will be shown how difficulties involved in obtaining input and output lines for direct use can be overcome. This will satisfy the initial demands of many microprocessor users. Where more complex strategies are required the interupt and handshake facilities of the PIA may need to be

incorporated.

Fig. 2. The typical procedure adopted by a user when configuring a PIA to operate in any one of its a v a i l a b l e modes.

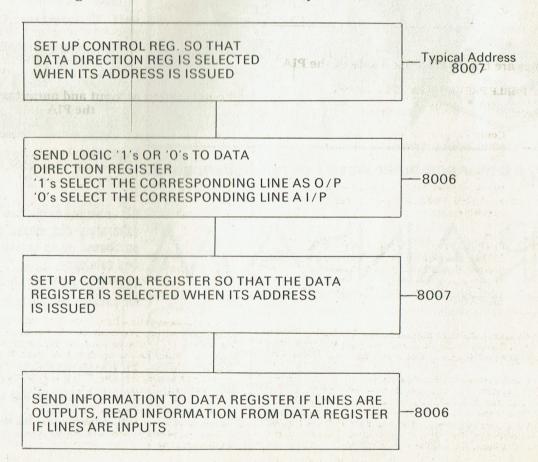

PIAs Simplified

The Internal Registers of the PIA

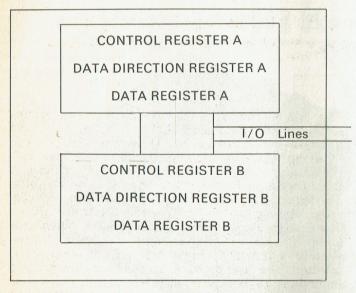


Fig. 1. The internal structure of a typical PIA. The Internal Register structure can be split into two distinct blocks each in turn consisting of a Control Register, Data Direction Register, and a Data Register. These Registers must be configured by the user to meet his requirements.

8 Output lines are needed on the B side of the PIA

POSSIBLE PREVIOUS PROGRAMMING

00 B7 STA A Send accumulator contents to Control F ister B. 80 80 As b2 = 0 the Data Direction Register B wi 07 07 accessed when address 8006 is next used. Load accumulator A with 1111 1111 (inbin FF B7 STA A Send accumulator contents to 8006. This 80 80 establishes PIA B side as outputs. (A 1 con ures 06 06 the corresponding line as an output.) Load accumulator A with 000 0100 04 04 B7 STA A Send accumulator contents to Control F ister B. 80 80 As b2 = 1, next time 8006 is addressed the I 07 07 Register is selected LDA A Load accumulator A with 0000 1111 as typ data	Code	mnemonic	Comments
B7 STA A Send accumulator contents to Control Fister B. 80 80 As b2 = 0 the Data Direction Register B wider accessed when address 8006 is next used. 86 LDA A Load accumulator A with 1111 1111 (inbin FF) 87 STA A Send accumulator contents to 8006. This establishes PIA B side as outputs. (A 1 control Fister B. 80 80 the corresponding line as an output.) 86 LDA A Load accumulator A with 000 0100 87 STA A Send accumulator contents to Control Fister B. 80 80 As b2 = 1, next time 8006 is addressed the Information of Informatio	86	LDA A	Load accumulator A with 0000 0000 (in binary)
ister B. 80 80 As b2 = 0 the Data Direction Register B wi 86 LDA A Load accumulator A with 1111 1111 (inbin FF FF B7 STA A Send accumulator contents to 8006. This 80 80 establishes PIA B side as outputs. (A I conversed to the corresponding line as an output.) 86 LDA A Load accumulator A with 000 0100 87 STA A Send accumulator A with 000 0100 88 STA A Send accumulator contents to Control Fixer B. 80 80 80 Register is selected 80 LDA A Load accumulator A with 0000 1111 as typedata	00	00	
07 accessed when address 8006 is next used. 86 LDA A Load accumulator A with 1111 1111 (inbin FF FF B7 STA A Send accumulator contents to 8006. This establishes PIA B side as outputs. (A I con ures 06 06 the corresponding line as an output.) 86 LDA A Load accumulator A with 000 0100 04 04 B7 STA A Send accumulator contents to Control F ister B. 80 80 As b2 = 1, next time 8006 is addressed the I 07 07 Register is selected LDA A Load accumulator A with 0000 1111 as typudata	B7	STA A	Send accumulator contents to Control Register B.
07 accessed when address 8006 is next used. 86 LDA A Load accumulator A with 1111 1111 (inbin FF FF B7 STA A Send accumulator contents to 8006. This 80 80 establishes PIA B side as outputs. (A 1 conures of the corresponding line as an output.) 86 LDA A Load accumulator A with 000 0100 of the corresponding line as an output.) 87 STA A Send accumulator A with 000 0100 of the corresponding line as an output. (A 1 conures of the corresponding line as an output.) 88 LDA A Load accumulator A with 000 0100 of the corresponding line as an output. (A 1 conures of the corresponding line as an output.) 88 LDA A Load accumulator A with 000 0100 of the corresponding line as an output. (A 1 conures of the corresponding line as an output.) 89 STA A Send accumulator A with 000 0100 of the corresponding line as an output. (A 1 conures of the corresponding line as an output.) 80 LDA A Load accumulator A with 000 0100 of the corresponding line as an output. (A 1 conures of the corresponding line as an output.) 80 LDA A Load accumulator A with 000 0100 of the corresponding line as an output. (A 1 conures of the corresponding line as an output.) 80 LDA A Load accumulator A with 000 0100 of the corresponding line as an output.) 81 LDA A Load accumulator A with 000 0100 of the corresponding line as an output.	80	80	As $b2 = 0$ the Data Direction Register B will be
FF FF B7 STA A Send accumulator contents to 8006. This establishes PIA B side as outputs. (A 1 converse of the corresponding line as an output.) 86 LDA A Load accumulator A with 000 0100 87 STA A Send accumulator contents to Control Fixer B. 80 80 As b2 = 1, next time 8006 is addressed the Incompanies of the Inco	07	07	
B7 STA A Send accumulator contents to 8006. This establishes PIA B side as outputs. (A I converse of the corresponding line as an output.) B6 LDA A Load accumulator A with 000 0100 B7 STA A Send accumulator contents to Control Fister B. B0 80 As b2 = 1, next time 8006 is addressed the I Control Fister is selected B8 LDA A Load accumulator A with 0000 1111 as typicate	86	LDA A	Load accumulator A with 1111 1111 (inbinary)
80 establishes PIA B side as outputs. (A I converse of the corresponding line as an output.) 86 LDA A Load accumulator A with 000 0100 87 STA A Send accumulator contents to Control Fister B. 80 80 80 As b2 = 1, next time 8006 is addressed the I Converse of the I C	FF	FF	
ures the corresponding line as an output.) LDA A Load accumulator A with 000 0100 LDA A Send accumulator contents to Control F ister B. Solution B	B7	STA A	Send accumulator contents to 8006. This
86 LDA A Load accumulator A with 000 0100 87 STA A Send accumulator contents to Control F 88 ister B. 89 So As b2 = 1, next time 8006 is addressed the I 80 Register is selected 80 LDA A Load accumulator A with 0000 1111 as type 4 data	80	80	establishes PIA B side as outputs. (A 1 configures
04 B7 STA A Send accumulator contents to Control F ister B. 80 80 As b2 = 1, next time 8006 is addressed the I 07 07 Register is selected LDA A Load accumulator A with 0000 1111 as typ data	06	06	the corresponding line as an output.)
B7 STA A Send accumulator contents to Control F ister B. 80 80 As b2 = 1, next time 8006 is addressed the I Register is selected 86 LDA A Load accumulator A with 0000 1111 as typedata	86	LDA A	Load accumulator A with 000 0100
ister B. 80 80 As b2 = 1, next time 8006 is addressed the I 86 LDA A Load accumulator A with 0000 1111 as typedata	04	04	
07 Register is selected 86 LDA A Load accumulator A with 0000 1111 as typedata	B7	STA A	Send accumulator contents to Control Register B.
86 LDA A Load accumulator A with 0000 1111 as typ	80	80	As $b2 = 1$, next time 8006 is addressed the Data
data	07	07	Register is selected
	86	LDA A	Load accumulator A with 0000 1111 as typical
0F 0F to be output	0F	0F	to be output
	A TOTAL CONTRACTOR OF THE PARTY		Send this data to 8006. This now acts as output
80 80 information	The same of the sa		
06 06			

This program sets up the B side of the PIA as 8 output lines then shows how to send out data along these lines. Address 8007 locates the Control Register with 8006 shared between the Data Direction Register and the Data Register.

Any data now sent from the microprocessor 8006 will act as output information. The code is the assembled version, written

in hexadecimal, of the instruction mnemonic.

The sequence involved in setting up the PIA for output and /or inputs can be generalised as shown in Fig. 2.

8 Input lines are required on the A side of the PIA

POSSIBLE PREVIOUS PROGRAMMING

Code	mnemonic	Comments
86	LDA A	
00	00	Control Register A is set so that
B7	STA A	when 8004 is addressed the Data
80	80	Direction Register is selected.
05	05	
86	LDA A	
00	00	The A side of the PIA is established
B7	STA A	by setting the Data Direction Register A
80	80	to 0000 0000
04	04	
86	LDA A	
04	04	Control Register A is set so that when
B7	STA A	8004 is next addressed the Data Register
80	80	is selected and the input data read
05	05	
B6	LDA A	Load into accumulator A the input data
80	80	from 8004
04	04	

Address 8005 locates Control Register A with 8004 shared between the Data Direction Register and the Data Register. The generalised diagram of figure 2 has been used to derive this program.

The 8 lines connected to the A side act as inputs to the microprocessor system. The data on these lines can be loaded into, say, accumulator A for further processing. The use of the LDA A instruction at the end of the previous program makes use of the extended addressing mode. The location 8004 is treated as a memory location and the instruction efficiently transfers the data present on the input lines to the accumulator.


A combination of input and output lines on side A of the PIA

code	mnemonics	Comments
86	LDA A	
00	00	Control Register A is set so that
B7	STAA	when 8004 is addressed the Data Direction
80	80	Register is selected
05	05	
86	LDA A	The A accumulator is loaded with
E0	E0	111 00000 (in binary). This is sent to
B7	STA A	Data Direction Register A to establish
80	80	b7, b6, b5 as outputs and b4, b3, b2, b1, b0
04	04	as inputs.
96	LDA A	
04	04	Control Register A is set so that when
B7	STA A	8004 is next addressed the Data Register
80	80	is selected.
05	05	

It is a characteristic of the PIA that individual lines in an 8-bit group can be programmed to be inputs or outputs. Normally input lines are grouped together and output lines are grouped together. In the following case five input lines and three output lines are required on the A side of the PIA. The three output lines are arranged to be on lines, 5, 6 and 7 with the input lines 0 to 4. (The most significant bit position is line 7).

The input data can read into accumulator A by using LDAA in extended mode on location 8004. Data can be output from an accumulator by using STA instruction on location 8004. Only the 3 most significant bits will be effective as outputs from the accumulator data.

From Science of Cambridge: the new MK 14.

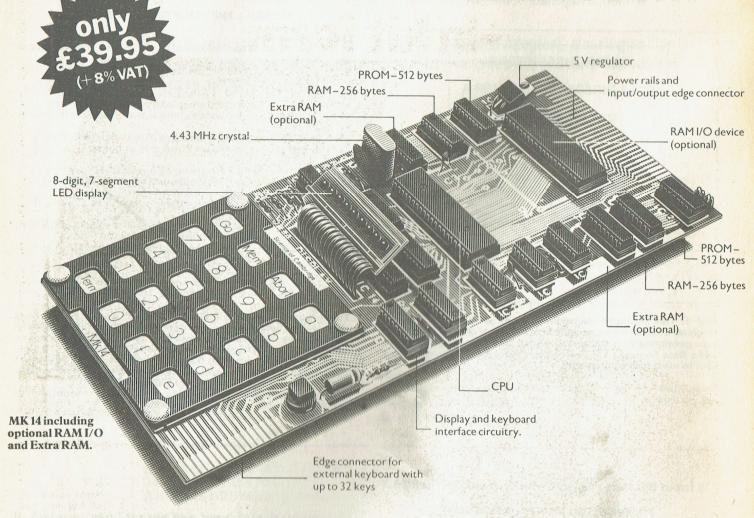

MK 14 — a complete computer for £39.95 (+8% VAT)

The MK 14 is a complete microcomputer with a keyboard, a display, 8 x 512-byte preprogrammed PROMs, and a 256-byte RAM programmable through the keyboard.

As such the MK 14 can handle dozens of userwritten programs through the hexadecimal keyboard. (20 sample programs are provided in the Manual – which also contains comprehensive building instructions, and instructions on program-writing.)

Yet in kit form (which can be assembled by any fairly experienced kit-builder), the MK 14 costs only £39.95 (+£3.20 VAT, and p&p).

But that's only the start ...

The memory capacity of the basic kit is surprisingly powerful – but every computer owner, from a schoolboy to a multi-national corporation, soon feels the need for more memory.

With the MK14, it's yours!

Optional extras include an additional 256-byte RAM, and a 16-line external input/output device (allowed for on the PCR) in the give a further 128 bytes of RAM.

And the next step?

The next step is to add your own peripherals!

The first could be a low-cost module which provides an interface with a standard cassette-recorder. This means you can use ordinary tape-cassettes for the storage of data and programs.

To get the best from this configuration, you could uprate your system with a revised monitor – consisting of 2 replacement PROMs, pre-programmed with sub-routines for the interface, offset calculation and single step, and single-operation data entry.

The second peripheral could be your own **PROM programmer and blank PROMs** to set up your own pre-programmed dedicated applications. (Fusible-link device guarantees program safety.)

All are available now to owners of MK 14—and remember Science of Cambridge keep you up to date *automatically* with advances in the MK 14 range. A TV interface device is already in the pipeline!

A valuable tool - and a training aid

As a computer, it handles operations of all types
—from complex games to digital alarm clock
functioning, from basic maths to a pulse delay
chain. Programs are in the Manual, together
with instructions for creating your own
genuinely valuable programs.

And, of course, it's a superb education and training aid – providing an ideal introduction to computer technology.

SPECIFICATIONS


MK 14

- * Hexadecimal keyboard
- * 8-digit, 7-segment LED display
- * 8 x 512 PROM, containing monitor program and interface instructions
- * 256 bytes of RAM
- * 4 MHz crystal
- * 4 MHz crysta * 5 V regulator
- * Single 8 V power supply
- * Space available for extra 256-byte RAM and 16 port I/O Edge connector access to all data lines and
- Edge connector access to all data lines at I/O ports

Optional Extras

- * Extra RAM-256 bytes
- * RAM I/O device

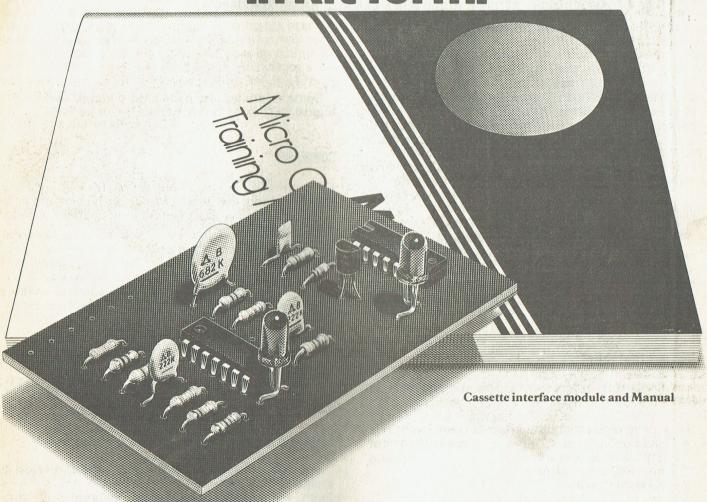Simplest, most advanced, most flexible microcomputer -in kit form.



- * Cassette interface module
- * Revised monitor
- * PROM programmer
- * Blank PROMS

Free Manual

Every MK 14 Microcomputer kit includes a Manual which deals with procedures from soldering techniques, through programming and use of RAM 1/O to interfacing with complex external equipment. It contains operational instructions and examples for training applications, and numerous programs including math routines (square root, etc.), digital alarm clock, single-step, music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 15 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings.

The MK 14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

How to get your MK 14

Getting your MK 14 kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK 14, return it to us within 14 days for a full cash refund.

Science of Cambridge

Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 ISN. Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Please send me the following, plus details of other MK 14 Standard Microcomputer Kit @ £43.55 (Extra RAM @ £3.88 (inc p&p.) RAM I/O device @ £8.42 (inc p&p.)	peripherals:
I enclose cheque/money order/PO for £Name	(indicate total amount.)
Address (please print)	

Beginning BASIC

Part 2 of our series looks at some of the more common BASIC statements.

THERE ARE SEVERAL dialects of BASIC in service at present, depending upon which machine you are programing for, and so we will make a start by looking at those parts of the BASIC language which are more or less universal.

The first thing to do is to define a few terms which we will be using throughout the rest of the series.

VARIABLE

THE RESERVE

A variable is a character (or sometimes group of characters) to which a numerical value may be assigned. The most common variable names and those which are used by most machines are the 26 single letters of the alphabet (A to Z). Other examples of variable names will be pointed out as we come across them.

ARITHMETIC OPERATOR

There are five common arithmetic operators in BASIC.

'=' - to be replaced by the value of (read as 'equals')

+'- addition operator equality operator

'-' - subtraction operator

'*' – multiplication operator'/' – division operator

Some machines have a sixth arithmetic operator '†' which means 'raised to the power of' (may also be written as '**').

COMPARISON OPERATORS

There are six common comparison operators.

'='-equals

'<' - less than

'>' - greater than

<=' - less than or equal to

(<>)' – not equal to (can also be $(\neq)'$)

'>=' - greater than or equal to

LOGICAL OPERATORS

00 6 8 6 5 mm.

There are two common logical operators.

'*' - logical AND (may be written as AND)

'+' - logical OR (may be written as OR)

Some machines also have a third logical operator – logical NOT (may be written as '~' or as 'NOT')

COMMAND

'Command' is the name given to keywords in BASIC which are used outside programs such as RUN, LIST, NEW etc. We will look at these in more detail later.

STATEMENT

The single instructions which go towards making up a program in BASIC are each called statements.

EXPRESSION

An expression is a collection of variables and/or numbers joined together by one or more arithmetic operators (so that 3*X+4, A-2 and A*(A+B)/(2-C) are all examples of expressions).

EQUATION

An equation is formed when an expression is assigned to a variable (so that $Y = 3* \times +4$, B = A - 2 and Q = A*(A+B)/(2-C) are all examples of equations).

There is one other thing which should be discussed at this time. It can be described as follows—

If we let X take a value of 2 then what value do you think will be assigned to Y in the following equation.

$$Y = 3 + X * X$$

If you thought the answer was anything other than 7 or 10, then you want to brush up on your maths. If you thought the answer was 7 then you are probably wondering where 10 came from and vice-versa. It all depends on whether you used a calculator or a computer to work it out. If you used a calculator then you would have worked it out like this—

$$Y = (3 + X)^*X$$
 or $Y = (3 + 2)^*2$

executing the operators as they occur and getting an answer of 10.

If, on the other hand, you used a computer, then you would have worked it out like this—

$$Y = 3 + (X*X)$$
 or $Y = 3 + (2*2)$

receiving an answer of 7. This may seem strange, but when computers do calculations they deal with the arithmetic operators in a certain order. First the computer scans the line left to right and performs all the multiplications and divisions as it encounters them; it then goes through again performing all the additions and subtractions that are left. The only way to alter the order of operations is to insert brackets where appropriate because the computer will work out the value of brackets before it does anything else and if there is more than one set of brackets one within another, it will work out the innermost brackets first.

So that, for example-

$$3+(2*(3+1*3))/(2+1)$$

has a value of 7 by the following reasoning.

The innermost brackets contain 3+1*3 which gives 6:3+(1*3): moving out to the outermost brackets we multiply this by 2 to give 12. This is one partial solution. We then move on to the last pair of brackets containing 2+1 and evaluate this as 3. That takes care of all the brackets and gives an expression which looks like this—

3 + 12/3

Division now comes before addition and this reduces to—

$$3+(12/3)$$
 or $3+4$

then the addition is done to give a final answer of 7.

Try evaluating the following expression—

$$7 + ((7*8)/2)/(((12+8)*2)/20)$$

When you have done this, try taking out all the unnecessary brackets (parentheses) without rearranging the order of the numbers (constants) and arithmetic operators so that the resulting expression gives the same result. The answers are given at the end of the article.

Certain facilities are required from any high level language, BASIC being no exception.

- 1. There must be a way of assigning values to any variables used in a program;
- 2. A method of outputting answers is also a must;
- The language must have branching capabilities and in particular conditional branching must be provided:
- Other facilities such as subroutines, string handling and some pre-defined functions are also useful and are usually provided.

LET

In BASIC the easiest way of defining a variable is to use a LET statement.

10 LET X = 3 20 LET Y = X - 2 30 LET T = T + 1

There are several things that you should notice here. Firstly, every instruction is preceded by a line number.

The computer, in executing a program in BASIC, does so in sequential line number order, starting with the lowest numbered line and going through to the highest numbered line except where a branching instruction is encountered in which case the next line number to be executed forms part of the instruction.

Secondly, the '=' sign in these instructions does not mean 'equals' in the normal sense of the word, but means 'to be replaced by the value of'. So that line 20, when translated into English, means something like this—


LET whatever exists now in the memory locations representing the variable Y 'be replaced by the value of' whatever exists now in the memory locations representing the variable X, minus 2.

This may seem a bit of a tongue twister (it would normally be read as "LET Y equal X minus 2") and has only been presented in this form to make line 30 a little easier to understand.

$$LETT=T+1$$

What does it mean?

Well, briefly, if the memory space for the variable T had a value of 2 before the execution of line 30, it would have a value of 3 after its execution. Got it? If not, refer back to the tongue twister, substituting the variables and constants from line 30 into line 20 where appropriate and read it through a couple of times until you have mastered this concept, because it is very important. You should now be able to see (if you read Part 1) that where the following flow chart box appears—

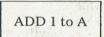

this could now be replaced by a box containing the following BASIC statement—

LET
$$A = A + 1$$

It is reasonable to point out at this time that on most machines which can run BASIC the LET statement is optional so—

10 LET
$$A = A + 1$$

and
 $10 A = A + 1$

are equally valid statements so that where, last month, we encountered the following—

To be continued ▶



we were (apart from line numbers) already considering BASIC statements.

GOTO

The simplest form of branching instruction in BASIC is the GOTO statement, an example of its use is seen below—

10 LET Y = 1 20 LET A(Y) = Y*Y 30 LET Y = Y + 1 40 GOTO 20

The format of the GOTO statement is quite straightforward. The keyword GOTO is followed by the number of the line to which you wish control of the program to be transferred. Therefore, this program segment would be executed in the following order—

10 20 30 40 20 30 40 20 etc

As well as the GOTO statement, a new type of variable has been introduced in this program segment; the single subscript variable (can be known as a one dimensional array) represented here by the variable name (A(Y). In Tiny BASIC as well as having single letters to represent variables (A, B, K, Y etc) you can also use variables of the following format—

A(1), A(2), A(10), A(50) etc

where A(1) is as different from A(2) as X is from Y (The ETI Triton uses the @ symbol for its one single subscript variable, the TRS-80 Level I uses A).

Can we think of a use for these new variables? Well, if we think back to last month's card shuffling routines, we came across the following—


Put Random Number R In Storage Location A

where A took values from 1 to 52.

If we say that A(1) is storage location 1 and A(2) is storage location 2 or, in more general terms, A(A) is storage location A, then we have a representation for what was last month a set of 52 storage locations. So it is now obvious that the above flow chart box could be replaced by the following—

A(A) = R

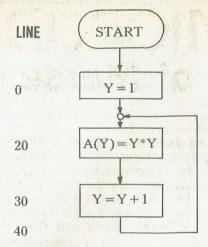Right! Let's go back to the program segment illustrating the GOTO statement.



This is its flow chart. We can see flow chart boxes representing lines 10, 20 and 30, but there is no box to represent the GOTO statement. It is merely represented by the box interconnection line which branches back to the connector between lines 10 and 20. While we are still on the subject, let's see what this program segment is actually doing (mentally executing a program without the aid of a computer is called DRY RUNNING a program).

Line 10 is the first line to be executed and all it is doing is assigning an initial value to the variable Y (in this case the value is 1). Now comes the line that might cause a bit of a problem.

20 LET A(Y) = Y * Y

If we think about the current value of the variable Y and substitute this value in the appropriate places, then what we end up with should make a lot more sense.

20 LET A(1) = 1*1

All this says is "write 1(1*1) into the memory space representing the variable A(1).

Now we pass on to line 30, which we have met previously, and this line adds 1 to the memory locations representing the variable Y; so Y now has the value 2.

Line 40 is the GOTO statement which tells us that the next line to be executed is line 20 again, and so we go back and re-write.

20 LET A(Y) = Y*Y

as

20 LET A(2) = 2*2

using the new value of Y so that we write 4(2*2) into the memory space representing the variable A(2). This process is now repeated for variables A(3) A(4) A(5) and so on. Unfortunately, we have included no method of stopping the program or of branching out of this loop as we have not yet covered such things, but bear with us and all will be revealed.

You may have noticed from the explanation so far given that this program segment is calculating the points for a graph of y=x and if we could look into the memory spaces representing the values of the variable A(Y) we would see the following—

 $A(1) \dots 1$ $A(2) \dots 4$ $A(3) \dots 9$

One of the unfortunate points about this program is that it is an infinite loop (ie it will go on for ever with increasing values of Y) so we will now go on to look at a method of controlling the number of times we go round the loop.

TO BE CONTINUED

MICRODIGITAL of Merseyside

WE SELL . . .

Science of Cambridge MK 14 Bearbags

Nascom

Rockwell AIM-65

Apple II

North Star Horizon

CASU

Panda

Chroma Chimes Monitel Chess/Draughts/Backgammon A superb selection of literature TI Programmer Calculator Multimeters, Soldering Equipment, Wire Wrap, etc.

Demonstrators of most of these on display

Opening hours: 9-5.30 Monday to Saturday

Friendly, expert staff always on hand!



CRODIGITAL LTD

and much more

25 BRUNSWICK STREET LIVERPOOL L2 0BJ

Tel: 051-236 0707

POSTAL OFFERS

10 quality C15 cassettes with library cases and special labels.....

£4.75

Science of Cambridge Socket Set 5x14 pin, 7x16 pin, 4x18 pin, 2x40 pin.

£3.89

Science of Cambridge power supply.....

£4.86

Universal microprocessor coding forms, pads 100 sheets each.....

above offers include V.A.T. and P. & P.

Please send me the items ticked above. I enclose Cheque/P.O. for.....

Access No..... Barclaycard No..... Please send me free, complete brochure. I enclose S.A.E. (please tick).

Address to:

MICRODIGITAL LTD., 25 BRUNSWICK STREET LIVERPOOL L2 0BJ.

Please allow 14 days for delivery.

ANNOUNCING THE M/I/C/R/O/S

IOIN THE MICRO REVOLUTION

£399 for a Z80 based microcomputer, built and tested Designed for educational establishments, personal computing and small business users

- Includes 1K monitor Eprom, 47 key solid state keyboard, video, TV, cassette and teletypewriter interfaces, serial i/o, 2 parallel i/o ports, 2K bytes RAM, power supplies and instrument housing.
- Connect to domestic TV or video monitor to complete the system
- 48 x 16 character video matrix
- 47 key contactless ASC11 keyboard
- Hard copy on teletypewriter
- 2 TTL compatible parallel i/o ports
- RS232 serial i/o port
- Load and dump programmes on unmodified cassette recorder



- Up to 16K byte mixed RAM and Eprom in table top housing
- Expandable up to 64K bytes
- Security locked power switch
- British designed and built
- Available in kit form for £360
- Credit terms available

PART OF THE MICRO REVOLTION

Prices exclusive of VAT and carriage

THE MICRONICS COMPANY

STATION ROAD TWICKENHAM MIDDLESEX



NewBear Computing Store



★ SYM-1

(Formally VIM-1)

The new 6502 micro from Synertek. Fully assembled and tested

Ex Stock @ £199.00

+8% V.A.T. Carriage £1.00

*NASCOM

Z80 BASED MICROCOMPUTER KIT

Ex Stock @ £197.50

+ 8% VAT £1.00. Carriage

Z80 CPU 2.5 MHz €6.99 Z80 P10 PS 2716 MIKRI €22.50 MIKBUG €13.65 £10.00 4116 £15.00 Z80 CTC PC €10.00 Interfacing I.C.'s Z80A CPU 4MHz SFF 96364 €20.50 Z80A PIO £11.55 MC 1488P £1.40 MC 1489P £1.40 Z80A CTC £11.55 MC 6800 €9.26 75150P €1.30 MC 6820 MC 6850 £4.63 £1.20 £2.30 75150N €6.74 75154 £3.61 £2.88 MC 6810 4N33 €1.95 MC 8602P AY-5-1013 €4.50 MC14536P £3.69 MC 3459 £2.53 6402 €4.50 €6.70 6571 SC/MP II £10.30 2501 £6.50 6502 £14.93 8080A £8.00 Buffers 81LS95 £1.30 Memories £1.25 81LS96 £1.35 81LS97 £1.30 2102-1 2102L-1 £1.30 £3.04 81LS98 €1.30 2112 £1.84 2513 £6.50 8T26 £1.60 **SWATBUG 8T95** £16.00 8T97 £1.60 2114 €8.25 74367 £1.30

24-HOUR TURNA-ROUND **ON ORDERS**

Please add 8% VAT to all prices. P&P 30p unless otherwise stated. Barclaycard and Access welcome. Overseas orders issued with Pro-Forma Invoice. Send for catalogue to Newbear Computing Store, Bone Lane. Newbury, Berks. Callers welcome Mon.-Sat., 9,00-5.30, but please phone us first on 0635 49223. New office — 2 Gatley Road, Cheadle, Cheshire. (Callers only). Telephone: 061-491 0134.

LIMITED SPECIAL OFFER! * N.L. 7001 V.D.U's.

(1977 Model)

- 12 TUBE
- FULL PROFESSIONAL ASCII KEYBOARD
- V24 INTERFACE AND CURRENT LOOP +
- * SWITCHABLE FULL AND HALF DUPLEX
- ALL METAL CASE

1.00

£9.95

€9.50

1.00

8080A Bugbook

BAUD RATE SWITCHABLE BETWEEN 50 AND 9600 BAUD



PLUS 8% VAT PLUS CARRIAGE

BEAR BAGS

- 1. 77-68 CPU PCB and Components £49.50
- 77-68 LED's and Switches £14.95 77-68 Power Supply €17.95
- 77-68 19 5u Rack and Backplane £26.70+
- 5. 77-68 4K Ram PCB and Components £74 00
- 6. 77-68 Mon 1 PCB and Components £50.00
- 7. 4K Ram Exorciser PCB and Components £71.50 8. 8K Ram Exorciser PCB and Components
- £160.00° Petitevid VDU Kit €85.00
- 10 £18.95 Kansas City Cassette Interface **UHF Modulator** £4.50
- 77-68 VDU PCB and Components 12. €69.50
- 13. 77-68 Mon 2 PCB and Components £t.b.a.
- 14. Prom Programmer PCB and Components £35.00
- 15. PROMVERTER (Enables a 2708 to be used instead of MIKBUG) £8.50

50p Postage and Packing unless otherwise stated + £1.50 Postage and Packing. £1.00 Postage and Packing.

Instant Freeze-Dried Con	puter Progra	mming in	basic.
By Jerald R. Brown	1000	€4.95	.75
My Computer Likes Me W	Vhen I Speak	in Basic	
AND THE PERSON NAMED IN COLUMN		€1.65	.30
Computer Programs that	Work	£2.40	.75
Basic Software Library	Volume 1:	£17.50	.50
	Volume 2	£17.50	.50
	Volume 3	€26.95	.50
	Volume 4	£7.95	.50
	Volume 5	€7.95	.50
	Volume 6	T.B.A.	.50
	Volume 7	€26.95	.50
NEW	BOOKS		
First Book of Kim		€7.00	.50
Z80 Microcomputer Hand	dbook	£7.25	.50
Using the 6800 Mircopro	ocessor	€6.25	.50
Micro 6502 Journal		£1.70	.50
Learning Basic Fast		€6.30	.50
How to Program Microco	mputers	£6.30	.75
Getting involved with you	ur Own Comp	uter	
		64 75	75

COMPUTER DESIGNS

		PAPP	
77-68 6800 Microcomputer	€7.50	.50	
Spare Diagram Set for 77-68	£1.50	.50	
WB-1 TTL Microcomputer	€6.50	.50	
Spare Diagram Set for WB-1	£1.00	.50	

FROM ADAM OSBOURNE ASSOCIATES

Payroll with Cost Accounting in Basic

Introduction to Microcomputers		
Volume O. The Beginners Book	£5.95	.50
Volume 2: Basic Concepts	£5.95	.50
Volume 2 Some Real Products June	1977 Revis	ion
	£11.95	1.00
8080A / 8085 Assembly Language Pr	ogramming	
	€6.95	.50
6800 Assembly Language Programmi	ing	
	€6.95	.50
Some Common Basic Programmes	£5.95	.50
6800 Programming for Logic Design	€5.95	.50
8080 Programming for Logic Design	£5.95	.50

SCELBI

Understanding Microcomputers & S	Small Cor	nputer
Systems	£7.56	.50
Scelbi 6800 Software Gourmet Guide	& Cookbo	ok
	£7.95	.50
Scelbi 8080 Software Gourmet Guide	and Cook	book
	€7.95	.50
8080 Standard Assembler	€15.95	.75
The Scelbi Byte Primer	£9.95	1.00
The 8080 Programmers Pocket Guide	€2.35	.30

ZILOG		
Z80 Technical Manual	€4.00	.50
Z80 PIO Technical Manual	£22.50	.50
MOTOROLA		
Understanding Microprocessors	€2.75	.30
M6800 Microprocessor Programmi	ng Manual	
	€4.50	.50

SYREX

Microprocessors C201	£8.00	.50
Microprocessor Interfacing Techniques	68.00	.50

M6800 Microprocessor Applications Manual

€6.95

.75

ETI BOOK SERVICE

computing-

BASIC: A Self Teaching Guide (2nd Edition) by ALBRECHT, R. L.

£4.50

Teach yourself the programming language BASIC. You will learn how to use the computer as a tool in home or office and you will need no special maths or science background.

Illustrating BASIC by ALCOCK, D.

This book presents a popular and widely available language called BASIC and explains how to write simple programs

£10.65

Gives a general overview of the technology design ideas and explains practical

£12.00

Applying Microprocessors

Follow up volume which takes you into the second and third generation devices

Intro to Microprocessors

£6.00

£7.50

£6.75

Explains the characteristics of the component.

How to Buy and Use Minicomputers and Microcomputers

Microprocessors — Technology, Architecture, and Applications by McGLYNN, D. R.

Microprocessor and Small Digital Computer Systems for Engineers and Scientists

£14.35

£6.10

£19.00

by BARDEN, W. Discusses these smaller computers and shows how they can be used in a variety of practical and recreational tasks in the home or business.

How to Program Microcomputers by BARDEN, W.

This introduction to the "computer-on-a-chip" provides a clear explanation of this important new device. It describes the computer elements and electronic semiconductor technologies that characterize microprocessors.

Outstanding for its information on real microprocessors, this text is both an introduction and a detailed information source treating over a dozen processors, including new third generation devices. No prior knowledge of microprocessors or microelectronics is required of the reader.

This book covers the types, languages, design, software and applications of micro-

An in-depth coverage of tv typewriters (tvt's)-the only truly low-cost microcomputer

and small-system display interface. Covers tyt terminilogy, principles of operation, ty configurations, memories, system design, cursor and update circuitry and techniques, hard copy, color graphics, and keyboards and encoders.

This book explains assembly-language programming of microcomputers based on the Intel 8080, Motorola MC6800, and MOS Technology MCS6502 microprocessors.

Programming Microprocessors by McMURRAN

Microprocessor Systems Design by KLINGMAN, E.

BASIC Programming

TV Typewriter Cookbook by LANCASTER, D.

by KEMENY, J. G.

A basic text.

Introduction to Microcomputers and Microprocessors by BARNA, A

A practical programming guide that includes architecture, arithmetic/logic operations, fixed and floating-point computations, data exchange with peripheral devices/compilers and other programming aids.

Provides the basic knowledge required to understand microprocessor systems. Presents a fundamental discussion of many topics in both hardware and software.

Microcomputer Based Design by PEATMAN, J. B.

£19.00

Microprocessors in Instruments and Control by BIBBERO, R. J.

£11.80

This book is intended for undergraduate courses on microprocessors.

Microprocessor and Microprocessor Systems by RAO, G. U.

£20.50

Introduces the background elements, paying particular regard to the dynamics a computational instrumentation required to accomplish real-time data processing tasks

A completely up-to-date report on the state of the art of microprocessors and microcomputers, written by one of the leading experts. It thoroughly analyzes currently available equipment, including associated large scale integration hardware and firmware

Basic BASIC by COAN, J. S.

An introduction to computer programming in BASIC language.

The 8080A Bugbook: Microcomputer Interfacing and Programming by RONY, P. H.

£7.60

Microprocessor Programming for Computer Hobbyists by GRAHAM, N.

£7.00 £6.20

£14.25

€7.50

The principles, concepts and applications of an 8-bit microcomputer based on the 8080 microprocessor IC chip. The emphasis is on the computer as a controller. 6800 Software Gourmet Guide and Cookbook

The Computer Book by HAVILAND, R. P.

8080 Software Gourmet Guide and Cookbook £7.80

Microcomputers, Microcomproesors, Hardware Software and Applications by HILBURN, J. L.

Understanding Microcomputers Gives the fundamental concepts of virtually all microcomputers

£7.60 £18.00

Complete and practical introduction to the design, programming, operation, uses, and maintenance of modern microprocessors, their integrated circuits and other components.

Building super calculators and minicomputer hardware with calculator chips

Microprocessors and Microcomputers by SOUCEK, B.

Here's a description of the application, programming, and interacing techniques common to all microprocessors. It concentrates on detailed descriptions of representative microprocessor families and includes explanations of digital codes, logical systems, and microcomputer organization. £6.25

Microcomputer Primer by WAITE, M.

Introduces the beginner to the basic principles of the microcomputers. Discusses the five main parts of a computer — central processing unit, memory, input/output interfaces, and programs. The important characteristics of several well-known microprocessors are given and a chapter is included on programming your own microcomputer.

Microprocessor/Microprogramming Handbook

€6.00

Authoritative practical guide to microprocessor construction, programming and applications.

HOW TO ORDER:

Make cheques etc payable to ETI Book Service. Payment in sterling only please. Orders should be sent to: ETI Book Service, PO Box 79, Maidenhead, Berks. All prices include P & P.





MICRO-COMPUTER NASCOM I for the HOBBYIST

As reviewed in E.T.I. Nov. '78: "Overall the Nascom is an excellent unit"

THE COMPLETE MICRO-COMPUTER AVAILABLE TO THE HOME CONSTRUCTOR

FEATURES

- Supplied in kit form for self-assembly
 Full documentation supplied
 Fully screened double-sided plated through hole printed circuit board
 Full 48 key keyboard included
 2K x 8 Ram
 1K x 8 monitor program in Eprom
 Powerful Mostek Z80 CPU
 16 x 48 character display interface to std un-modified T.V.

- T.V. display memory mapped for high speed access
 On board expansion to 2K x 8 Eprom
 On board expansion for additional 16 I/O lines
 Memory may be expanded to full 60K (plus 4K existing on board)

SOFTWARE FEATURES

- 1K x 8 monitor program providing 8 operating commands, supporting Mem examine/modify, tabulate, copy, break, single step execute tape, load, tape dump.
- Reflective monitor addressing for flexible monitor expansion through user
- programs

 Monitor sub-routines include delay ASCII coding, binary to hex conversion, clr screen, scroll up, string print, cursor shift and many others.

EXPANSION

MEMO	RY	K	17	S	(i	no	du	S	iv	e	al	11	na	rc	In	a	re)											
																													£85.00
16K																							1						£140.00
32K	4.					1		P.																					£200.00

NEW "B-BUG" extended monitor in 2K of EPROM. Fully software compatible with NASBUG, supporting additional features.—
Full keyboard shift for all 128 characters, full cursor movement routines, Read

And Write commands (fast tape load and dump), H and N commands (for inserting ASCII code directly into programme). Arith. command (for calculating relative jumps), Generate command (for automatic programme start). Intelligent copy (for non-destructive re-location of DATA), Random, block handling, ASCII to BCD and BCD to ASCII routines and many more. 2 EPROMS + full documentation — £21.66.

* S.a.e. for full expansion details.

OTHER HARDWARE

	3A power supply for up to 4K expansion £19.90
*	8A power supply for larger than 4K expansion
*	Expansion card frame £29.50
*	Programming manual £4.00
*	Hardware & software manuals (supplied in kit) £3.00

Export Trade, Government and Educational Enquiries Invited

Add VAT at 8% on all items except manuals



Demonstrations Continuous at our Store



Construction Manuals Separately £3.00

Complete Kits NOW IN STOCK £197.50 +VAT 8% POST PAID

Sole Appointed London Stockists



HENRY'S RADIO 404 Edgware Rd. London W2 PHONE (01)723 1008

COMPUTER SYSTEMS LIMITED



DON'T FORGET SPECIAL OFFER £10 discount on orders dated before Dec. 12. So hurry!

The new low cost VDU - Tangerine 1648 (See page 16, ETI, Oct. '78 for feature details)


ORDERING INFORMATION

The normal KIT price is £139.86, which includes postage, packing and insurance and VAT @ 8%. HOWEVER, as an introductory gesture we are discounting this price by £10, for all orders received postmarked BEFORE 12th December, 1978.

If you require further information, send an A4 sized self-addressed envelope. If you wish to purchase a kit please send a cheque or money order made payable to

TANGERINE COMPUTER

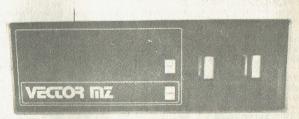RIVERMILL LODGE, LONDON ROAD, ST. IVES, CAMBS. PE17 4BR Tel. St. Ives (0480) 65666



THE TOTAL SOLUTION FROM

OF COURSE!

Now Almarc & Vector Graphic offer the complete solution to your computing needs for £2300.00°. The Vector MZ needs only the addition of a V.D.U. and it's ready to go. Completely assembled and fully tested, the Vector MZ offers the following features as standard:-

- S-100 bus 4 MHz Z80A processor
- 158 instructions
- Two quad density Micropolis floppies over 630k bytes on line
- Serial port
- Two parallel ports 32K static ram
- 12K prom/ram board with extended monitor
- Extended disc Basic

Simply connect your peripherals (Elbit V.D.Us & Centronics printers are available from Almarc) and you're up and running and, because the MZ uses the S-100 bus, you can plug in a massive range of add-on units.

Ring or write for a demonstration to:-

ALMARC DATA SYSTEMS LTD.

29 Chesterfield Drive Burton Joyce, Nottingham Tel: 0602 248565

*Discount terms available

MICROBIOGRAPHY THE 8080

This month we begin a series of in-depth interviews with various CPU celebrities—starting with the device used in the TRITON.

THE INTEL 8080 has become an industry standard. For those of you with mainframe computing experience, it is the FORTRAN of processors — vast amounts of software are available for it and many people have experience of it.

It was for this reason that it was used in the ETI TRITON. Not only does it have its own software following, it will also run programs written for the earlier 8008 and the much more advanced Z-80 will (with a little help, no doubt) run 8080 programs, although writing for the Z-80 is more demanding.

What we hope to provide in this series of articles is enough information on a number of processors to enable the reader to decide which is best for a particular application.


Registers

Not all of the registers shown on Fig. 1 are available to the programmer. The ones which are available are:
The accumulator;

registers B, C, D, E, H and L; the stack pointer and the program counter.

The accumulator

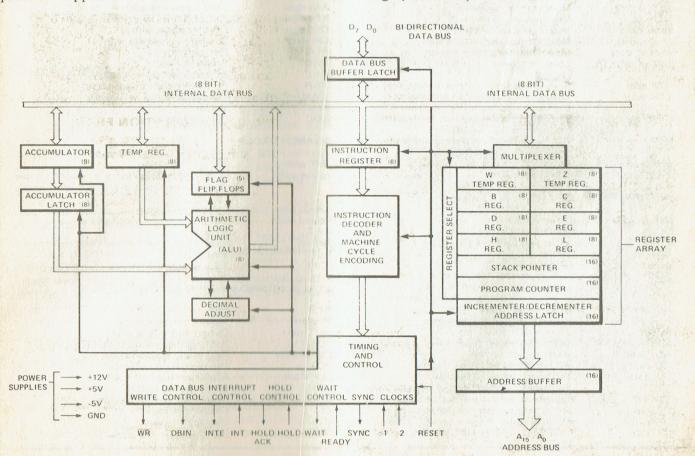This is the scratch-pad of the CPU. Most instructions allow you to prod the accumulator in some way. The state of the contents of the accumulator affects the flags (see below).



Registers B, C, D, E, H and L

The CPU allows you to move data from register to register in this set but if you want to do anything clever to the data you have to put it into the accumulator.

Register pairs B&C, D&E, H&L and the stack pointer

Some of the instructions allow you to treat some pairs of registers as one 16-bit register (each individual register holds 8 bits). The allowable pairs are shown above. Most of these instructions can also be used on the stack pointer, which holds 16 bits.

Register pair H&L

Instructions which refer to a particular byte of memory usually do so by means of the H&L registers. The memory location is held in these registers (most significant 8 bits in the H register).

Program counter

This points to the position in the program which the CPU is at. By changing this (via jump instructions), the CPU can be made to jump to a different part of the program.

Stack pointer

One of the nice things about the 8080 is its ability to keep a stack in external memory automatically.

What is a stack, you ask?

A stack is like a stack of magazines. When you put data 'onto' the stack, the CPU will add 1 to the stack pointer and then put the data into the memory location which the stack pointer is 'pointing' at (i.e. the top of the pile). When you take data off the top of the stack, the CPU will copy it from the stack pointer location and then subtract 1 from the stack pointer.

This is very useful for interrupts, during which the CPU is asked to stop what it is doing and go and do something else. When this happens the CPU can save all the register contents by putting them onto the

THE 8080 INSTRUCTION SET

r stands for register eg A register rp stands for register pair, eg b and C registers 'data' means the contents of the second or second and third bytes of the instruction M stands for memory whose address is in the H and L registers

DATA TRANSFER GROUP

	[1] : [1] - [1]
MOV r1, r2	Move register to register
MOV M, r	Move register to memory
MOV r.M	Move memory to register
MVI r. data	Move immediate (to register)
MVI M, data	Move immediate (to memory)
LXI rp, data 16	Load immediate (to register pair or to stack pointer)
STA addr	Store direct (accumulator to memory)
LDA addr	Load direct (memory to accumulator)
XCHG	Exchange H&L with D&E registers
STAX rp	Store accumulator indirect (with address in registers B&C or D&E)
LDAX rp	Load accomulator indirect (with address in registers B&C or D&E)
SHLD addr	Store H&L direct
I HI D addr	Load H&L direct

ARITHMETIC GROUP

INR	Increment register
DCRr	Decrement register
INRM	Increment memory
DCR M	Decrement memory
ADDr	Add register to A
ADCr	Add register to A with carry
SUBr	Subtract register from A
SBBr	Subtract register from A with borrow
ADD M	Add memory to A
ADC M	Add memory to A with carry
SUB M	Subtract memory from A
SBB M	Subtract memory from A with borrow
ADI data	Add immediate to A
ACI data	Add immediate to A with carry
SUI data	Subtract immediate from A
SBI data	Subtract immediate from A with borrow
INX rp	Increment register pair (or stack pointer)
DCX rp	Decrement register pair (or stack pointer
DAA	Decimal adjust A (gives two BCD digits)
DAD rp	Add B&C, D&E or H&L to H&L

LOGIC GROUP

ANAr	AND register with A
XRAr	EXCLUSIVE-OR register with A
ORA r	OR register with A
CMPr	Compare register with A
ANAM	AND memory with A
XRAM	EXCLUSIVE OR memory with A
ORAM	OR memory with A
CMP M	Compare memory with A
ANI data	AND immediate with A
XRI data	EXCLUSIVE-OR immediate with A
ORI data	OR immediate with A
CPI data	Compare immediate with A
RLC	Rotate A left
IRRC	Rotate A right
EAL	Rotate A left through carry
FIAR	Rotate A right through carry
CMA	Complement A
STC	Set carry
CMC ant	Complement carry
PIDANCH CROUP	

BRANCH GROUP

JN1P addr

Joond addr	Jump on condition specified (carry, no carry, zero, no zero, positive, minus, even or odd parity)
CA LL addr	Call unconditional
Coond addr	Call on condition specified (see above)
RET	Return
Recond	Return on condition specified (see above)
RST	Restart
PCHIL	H&L to program counter
STACK, I/O	AND MACHINE CONTROL GROUP

Jump unconditional

HLI	Hait
IN port	Input (from port to A)
OUT port	Output (from A to port)
PUSIH rp	Push register pair on stack (in memory)
PUSH PSW	Push A and flags on stack
POP rp	Pop register pair off stack
POP PSW	Pop A and flags off stack
XTHL	Exchange top of stack with H&L
SPHL.	Move H&L to stack pointer
EI	Enable interrupts
DI	Disable interrupts
NOP	No op

THE 808

stack. When the interrupt is over it can then read them back off the stack and go back to what it was doing.

This facility is also useful for subroutine calls.

Flags

A flag in this context is nothing to do with patriotism. It is one bit of a register which signals a particular condition.

There are five flags in the 8080's ALU: zero, parity, carry, auxiliary carry and sign.

All of them reflect the state of the data in the accumulator. They are accessed by means of the conditional jump class of instruction.

The interrupt enable flag (see Fig. 2) can also be

set or reset by machine code instruction.

Instruction Set

Table 1 shows the 8080 instructions set.

The POP and PUSH instructions take data from and put data onto the stack, respectively.

The rotate class of instructions make the accumulator act like a shift register.

Increment and decrement add or subtract 1 from

the relevent registers, respectively.

The NOP instruction is useful where there may be some changes in the program — to save shifting the rest of it to get more room.

Addressing Modes

The different ways in which the data following the machine code instruction byte can yield data are called 'addressing modes'. The ones which the 8080

Immediate mode: Bytes 2 and/or 3 of the instruction contain the 8 or 16 bits of data to be used.

Direct addressing: Bytes 2 and 3 contain the address of the data in memory.


Register addressing: The instruction specifies which register the data is in.

Register indirect addressing: The instruction specifies a register pair (giving 16 bits) which is the address of the data in memory.

These modes are implicit in the description of the instruction set in Table 1 but the list shown above gives a useful overview.

Summary

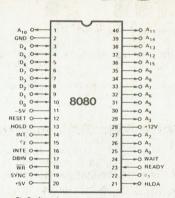The 8080 is a good general purpose CPU with adequate arithmetic operations. The instruction set is easy to follow and easy to use. The stack facility is nice, slightly marred by the lack of any single-byte stack instructions.



A0-A15: Address bus. Provides the address of a required memory location or I/O device number. Least significant bit = A0.

D0-D7: Tri-state bidirectional data bus. Least significant bit = D0.

SYNC: Indicates the beginning of each machine cycle.

DBIN: Indicates that the data bus is ready for data input.

READY: Tells the CPU that valid data is on the data


bus, ready for input. If requiring data, the CPU will enter a 'wait' state until READY goes high. WAIT: Active when CPU is in 'wait' state.

WR: Shows that the data bus carries valid output.

HOLD: Request to CPU to stop what it is doing and make the address and data busses high impedance. HOLDA: High when CPU acknowledges the HOLD request and goes into a HOLD state.

INTE: INTE high means that the CPU will accept maskable interrupts. The state of INTE can be changed by the relevant machine code instruction. INT: Interrupt request. Asks the CPU to jump to the relevant interrupt address.

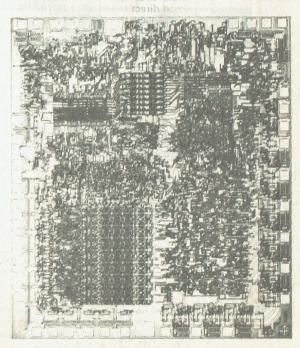RESET: Clears the program counter, INTE and



Solve the clues shown and enter them on the form below as though it were a cross-word

but you will be entering numbers. In some cases leading zeros must be supplied.

Some of the clues are tough — but they are not tricks and those which you cannot answer from your head will be available in common reference books, from past issues of ETI, in particular the November issue featuring the TRITON. Note: Any arithmetic must be performed with TRITON's TINY BASIC's restrictions in mind.

RULES

This competition is open to all U.K. and Northern Ireland readers of Electronics Today International except employees of the magazine, their printers, distributors, employees of TRANSAM, and anybody associated with the competition.

All entries must be on the coupon cut from the magazine, photostats are not acceptable. As long as the correct coupon is used, readers may submit as many entries as they wish.

Completed entries should be sent to 25/27 Oxford Street, London W1R 1RF and marked Computing Today Competition.

The Prize will be awarded to the first correct entry drawn after the closing date. No correspondence can be entered concerning the competition. It is a condition of entry that the judges' decision in all matters is regarded as final.

The winners will be notified by post. The answers and the names of the prizewinners will appear in a future issue of E.T.I.

18	0	28	0		3		4	
		er eus		5	5	6	6	77
		88	95	5		007		Lewiski
10	11	9	6		12	-	13	
			14 CAS	00	Z			
15	8	16	0		17	18	ra.	19
		10 Fine		20		M. C. K.		202
21	22	Those are	23	1		200		
	4		后		24		POLITY NO.	

ACROSS

- 1. TRITON'S inteligent MPU
- BASIC's largest number
- 8. Tick-tock UART's clock
- 10.4K
- 12. 100*11+27+5/6
- 14. Secret agent
- 15. Motorola's best known MPU
- 17. Controlling influence for TRITON
- 20. Bit of a reverse (see16) 21. Needle in a STAC
- 24. Remember this IC

DOWN

- Tick-tock TRITON's clock
- Intel's programable interrupt controller
- 3. To to the fife.

- 4. No. of add. lines
- 5 Put a hex on 065 (Octal)
- Operate on this amp.
- The first is there, repeat for the rest
- Green blue red (resistively speaking)
- 11. We've just ate here
- 12. Give us a ring 13. 24 across with nothing removed
- 41/2+100*6-5
- 16. Backward 6 (in binary)
- 17. In control of TRITON
- 18. S.F. classic
- 19. Any port in a storm
- 20. Hecks its 4 down
- 22. Logic series
- 23. 8 bit MPU's max. address

Name	
Address	

CLOSING DATE DECEMBER 31st 1978

MEMORIES

2112 (256 x 4 Static RAM)

21L02 (450ns)

(1K x 1 Static RAM) 21L02 (250ns) £1.60

2114 (1K x 4 Static RAM)

£7.70

£1.07

4027 (300ns, equiv 2104)

£2.02

(4K x 1, 16 pin, Dynamic RAM) 5208 (equiv. 2107) £3.21

(4K x 1, 22 pin, Dynamic RAM) 4116 £18.00

(16K x 1, Dynamic RAM) 2708 £7.87

(1K x 8 UVEPROM)

8080A (CPU) £7.45

81LS95 (Buffer TriS) 75p 81LS96 (Buffer TriS) 75p

All VAT inclusive 35p for p&p orders under £5 Please write for discounts over 100 pieces

PET CORNER

Lotus now carry an exciting range of products for your CBM PET.

24K Memory Expansion

- Mounts inside PET
- Runs from PET's own power supply
- Takes 10 minutes to fit
- ★ Includes memory test program
- ★ 6 month warranty

£399 inc. VAT & P&P

MUSIC BOX

Turns your PET into a programmable musical instrument. You can record and play up to 90 pages, 16 notes per page, change tempo, key, etc.

£37.50 inc. VAT & P&P

T.I.S. WORKBOOKS

A set of 5 workbooks to give you a full understanding of all the ins and outs of your PET more fully than any previous manuals.

£15.95 per set. inc. P&P Dustcover £17.95 inc. VAT & P&P

Lots of software and other goodies. , Send large SAE.


OTUS

The Age of Affordable Personal **Computing Has Finally Arrived**

Ohio Scientifics

Superboard II

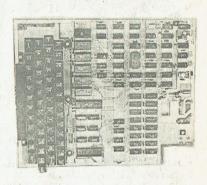Full 8K basic and 4K user RAM £284.95 **Built and tested**



Ohio Scientific has made a major breakthrough in small computer technology which dramatically reduces the cost of personal computers. By use of custom LSI micro circuits, we have managed to put a complete ultra high performance computer and all necessary interfaces, including the keyboard and power supply, on a single printed circuit board. This new computer actually has more features and higher performance than some home or personal computers that are selling today for up to \$2000. It is more powerful than computer systems which cost over \$20,000 in the early 1970's.

This new machine can entertain your whole family with spectacular video games and cartoons, made possible by its ultra high resolution graphics and fast BASIC. It can help you with your personal finances and budget planning, made possible by its decimal arithmetic ability and cassette data storage capabilities. It can assist you in school or industry as an ultra powerful scientific calculator, made possible by its advanced scientific math functions and built-in "immediate" mode which allows complex problem solving without programming! This computer can actually entertain your children while it educates them in topics ranging from naming the President of the United States to tutoring trigonometry all possible by its fast extended BASIC graphics and data storage

The machine can be economically expanded to assist in your business, remotely control your home, communicate with other computers and perform many of the other tasks via the broadest lines of expansion accessories in the microcomputer industry

This machine is super easy to use because it communicates naturally in BASIC, an English-like programming language. So you can easily instruct it or program it to do whatever you want, but you don't have to. You don't because it comes with a complete software library on cassette including programmes for each application stated above. Ohio Scientific also offers you hundreds of inexpensive programs on ready-to-run cassettes. Program it yourself or just enjoy it, the choice is yours.

Standard Features

- Uses the ultra powerful 6502 microprocessor
- 8K Microsoft BASIC-in-ROM Full feature BASIC runs faster than currently available personal computers and all 8080-based business com-
- 4K static RAM on board expandable to 8K
- Full 53-key keyboard with upper-lower case and user programmability
- Kansas City standard audio cassette interface for high reliability
- Full machine code monitor and I/O utilities in ROM
 Direct access video display has 1K of dedicated memory (besides 4K user memory), features upper case, lower case, graphics and gaming characters for an effective screen resolution of up to 256 by 256 points. Normal TV's with overscan display about 24 rows of 24 characters, without overscan up to 30 x 30 characters.

- Available expander board features 24K static RAM (additional mini-floppy interface, port adapter for printer and modem and OSI 48 line expansion interface
- Assembler/editor and extended machine code monitor

Commands	LIST	NEW	NULL	RUN	
CLEAR GOTO NEXT REM	DATA GOSUB ONGOTO RESTORE	DEF IFGOTO ONGOSUB RETURN	DIM IFTHEN POKE STOP	END INPUT PRINT	FOR LET READ
Operators -, +, *, /		D, OR, >, <,		=, =	

			RANG	E 10 ⁻³² to 1	0+32
Functions ABS(X) LOG(X) SPC(I)	ATN(X) PEEK(I) SQR(X)	COS(X) POS(I) TAB(I)	EXP(X) RND(X) TAN(X)	FRE(X) SGN(X) USR(I)	INT(X) SIN(X)
String Funct ASC(X\$)	tions CHR\$(I)	FRE(X\$)	LEFT\$(X\$,I)	LEN(X\$)	MID\$
RIGHT \$ (X\$,I)		STR\$(X)		(X\$,I,J VAL(X\$)

Plus variables, arrays and good editing facilities.

Fully built and tested. Requires only +5V at 3 amps and a videomonitor or TV and RF converter to

At this price there is going to be an enormous demand for Superboard II and supplies are going to be extremely limited. Lotus Sound is expecting first deliveries from the States in mid-December and orders will be treated strictly in the order they arrive, so post off today if you want to avoid long

4 MORGAN ST., LONDON E3 5AB

(Mail Order only)

Statem statement	To: LOTUS SOUND 4 MORGAN ST., LONDON E3 5AB	note factorial
Statement Streets II	Please send me Ohio Scientific Super Computer(s) I enclose cheque/PO for £	
NAME AND ADDRESS OF	Name	
second named day		
1		

Full 128 character set with ROM encoder (Upper and lower case + control shift).

Fully TTL - compatible - power requirements + 5v-12v. Supplied with full technical data, code chart, pin connections, circuit diagram and application notes.



+£1.50 p&p + 8% VAT (mail order total £66,42)

SELF-SCAN ALPHANUMERIC PANEL DISPLAY

16/18 position display with 64 character repertoire, 5×7 dot matrix. Input 6-bit BCD-code, power requirements +5v, -12v. Character size 0.40" × 0.28". Overall dimensions 8½" × 2½" × 1½". Supplied with full technical data. Price £55.00 +75p P&P+8% VAT (Mail order total £60.21).

BALL MIRATEL VIDEO MONITOR

9" diagonal P4 phosphor 9" diagonal P4 phosphor tube. Bandwidth 12 MHz (-3dB). Input voltage 220V 50/60 Hz 24V. Output voltage +15V DC (short circuit protected) +12kV DC; 12.6V rms. Supplied complete with high & low voltage power supplies, amplifier, and attractive moulded plastic housing including space for keyboard. Price space for keyboard. Price £95.00 + carriage + VAT.

PURCHASE - MITE HAZELTINE VISUAL DISPLAY UNIT



BRAND NEW SURPLUS ONLY £75

(Mail'order total £84.78)

standard reversible typewriter ribbon. Prints standard 64-ASCII character set on 8 ½" paper (80 characters per line, 6 lines to the inch). Maximum speed 11 cps. Power requirements 115VDC. Compact, light-weight unit 9% lbs, 12" × 9" × 2%." Supplied complete with +£3.50 P &P +8% VAT full technical manual. We also specialise in: DEC minis—PDP8 and PDP11 processors, add-on memory, peripherals and spares. Hard copy terminals—ASR 33 and KSR 33 Teletypes, Data Dynamics 390, Texas Silent 700. Send for complete lists.

ELECTRONIC BROKERS LTD

49-53 Pancras Road, London NW1 2QB Tel: 01-837 7781. Telex: 298694.

123P Alphanumeric

printer mechanisms

Solenoid-operated page printer using

Teletype Compatible

56-STATION ASCII KEYBOAF

- 12" Diagonal Screen
- TTY Format Keyboard
- 12 lines of 80 characters
- * 64 ASCII Character Set
- * 5×7 Dot Matrix
- Switch-selectable Transmission Speeds up to 9600 baud
- Switch-selectable Parity * Standard CCITT V.24 Interface



MODEL H-1000 PRICE £350 Also available:

Model H-1200: Specification as for H-1000 except 24 lines of 80 characters displayed. Price £425.00 + carriage + VAT.

Model H-2000: Buffered/Editing model with direct cursor addressing, dual intensity video, and detachable keyboard with separate numeric and edit clusters. 27 lines of 74 characters. Price £495.00 + carriage + VAT.

A copy of trading conditions supplied on request.

A more interesting way to lear



what is a croprocess

> If you are considering buying a Microcomputer, Development System, or just want to learn more about this exciting technology, then this short introduction to Microprocessors is for you. Comprising of a 72-page book keyed to over two hours of cassette tapes the many aspects of Microprocessors are explained, including Binary and Hexadecimal counting. Internal structure. Operation. Programming Techniques. Devising a program., etc. Learn at your own pace with this valuable addition to your reference library.

To Technical Book Services Maidenhead, Berks SL6 2EG

ORDER FORM

Please send me....copy/copies of What is a microprocessor? @£10.75 each inclusive. I enclose remittance £.....

Name (Print Please)

Address.

Registered office 21, Mincing Lane, London EC1 Registered No 12225

EPROM Programmer

Program your own 2708 EPROMS by connecting this project up to your systems serial port.

MOST HOBBYISTS now use EPROMs (Eraseable PROMs) of the 2708 type for the various firmware in their systems. 2708s are not now as expensive as they used to be, and have the advantage of allowing you to correct those inevitable bugs in your own programs or reuse the EPROM for some completely dif-

ferent program.


That's all very well, I hear you say, but I don't have a way of programing 2708s. Plus, commercial EPROM programmers are too expensive for me to justify since I only program one EPROM a month. Thanks to reader N. D. Hammond (and of course ETI) your troubles are over. Here is an inexpensive, nay, cheap, 2708 programmer suitable for individuals or impecunious clubs.

The programmer is, in fact, slightly different from the original design submitted to us by Mr Hammond; we have replaced some TTL in his design with CMOS and added a data time-out synchronisation facility, on which more later.

Design Features

The objectives of the original design were simplicity of construction and operation, and low cost. Another requirement which must be met is simplicity and versatility of interfacing — one of our bigger headaches is the fact that everyone's system seems to be different.

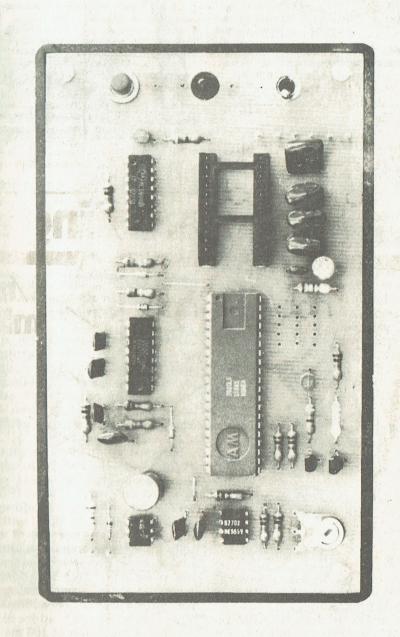This project meets these objectives very well. The interface to the user's computer is serial, i.e. through a 20 mA current loop. As a bonus, the UART and a couple of one-shots provide all the necessary timing signals, so the component count is low and cost is low.



A useful by-product of our switch to a completely CMOS design was a spare gate, which we put to good use in providing a 'synchronisation' facility. The idea is that if a supply glitch or noise causes the UART to miss a byte of data, so that the 2708 addressing is out of step with the desired addressing, a ¼ second pause at the end of each cycle will reset the 4040 to zero. This means that only that cycle will be affected and subsequent cycles will be correct, increasing the programmer's tolerance to glitches.

There is one slight penalty that has to be paid — at 300 baud, it will take about 70 minutes to output all 1024 addresses 125 times. This is by no means brilliantly fast compared to the theoretical minimum programming time of 104 seconds but it is a lot better than the several days that would be required by a com-

mercial firm.

Mr Hammond originally supplied software for the 8080, but our tests of the circuit were done on a MEK6800D2, for which we have written a routine, reproduced here. Our routine incorporates a time delay of approximately 1/4 second at the end of each run through the 2708 addresses, in order to take advantage of the time-out synchronisation feature. Mr Hammond's 8080 program does not include this facility, but it is easy to add a time delay loop which decrements (say) the BC pair using the DCX instruction. We hope to give this program next month (so much to do, so little time, sigh!), but Mr Hammond's routine should work with no modification.

Adjustment


Before adjusting the oscillator frequency first fit the links which set the start-stop bit arrangement of UART.

Now with power connected adjust RV1 until IC2 is operating at 4800 Hz.

The 2708

At this point we digress to describe the 2708 and the steps involved in using and programming it.

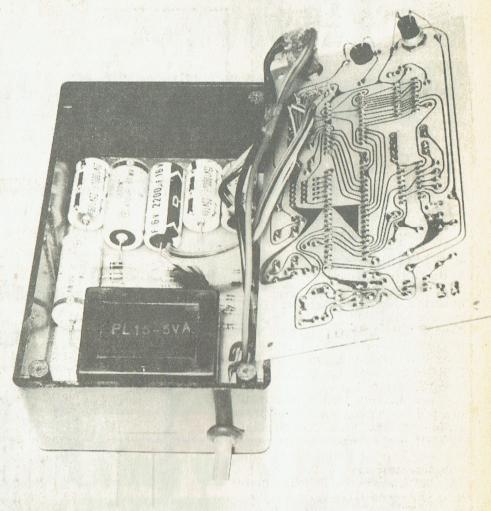The device is a static 8192 bit EPROM organised as 1024 x 8. It is packaged in a 24 pin DIP with a



quartz window which allows the data stored in the memory to be erased by exposure to ultra-violet light.

Reading the device is quite straightforward. The appropriate address is applied at the ten address pins, the chip select pin is taken low and after the appropriate access time (120ns from CS or 450ns from address select) the data is available

at the eight output pins.

Fortunately, and in contrast to its predecessors, the 2708 is also simple to program. The chip select pin is taken to the 'write enable' level of +12 V and the applied address is cycled from 000H to 3FFH with the appropriate data applied at each address. After the data and address lines have settled at each address, a 26 V pulse of 0.1 ms to 1 ms duration is applied at the programming pin. The entire cycle of 1024 addresses is repeated until each address has received a minimum of 100 ms program pulse time.

Erasure is the simplest operation of all. The window is uncovered and the chip placed an inch or so away from an ultra violet tube. After half an hour or so, the memory is fully erased (to all '1's) and is ready for re-programming.

Operation

A fully erased EPROM has every bit set to the '1' state. Programming sets selected bits to '0'. It follows that a 2708 can be reprogrammed without erasing if there are no cases where a bit must be changed from '0' to '1', otherwise the device must be erased by exposure to ultra violet light. Any 'germicidal' UV tube is suitable for erasing. The chip(s) should be placed about an inch or so from the tube and left for at least half an hour to ensure complete erasure.

To program the device, the pattern to be written should be available in RAM. The programmer

EPROM Programmer

Parts List

Main board

RESISTORS	
(All 1/2W 5%)	
R1,17	180R
R2,3,6,11,	
13,15	10k
R4,5,12	1ko
R7	4M7
R8	180k
R9	100k
R10	470R
R14	33k
R16	47R

POTENTIOMETER

RV1 25k

CAPACITORS

CI	8n 2 polyester
C2-C4,6,7	10n polyester
C5	33n polyester
C8,9,11,12	100n polyester
C10	100u 25V electrolytic
C13	10u 35V electrolytic

SEMICONDUCTORS

SEIVITON	DUCTURS
IC1	4N33 Opto coupler
IC2	555
IC3	MM5303 UART
IC4	4049
IC5	4040
Q1	PN3638
Q2	BC548
03	BC558
Q4	BC548
D1-D4	1N914
LED1	


MISCELLANEOUS


PCB as pattern 24 pin IC socket Push button

Plastic box 158x96x50mm

Parts List

RESISTO		DIODES	4844004
(All 1/2W 5	5%)	D1-D6	1N4004
R1	1k	ZD1	27V 1W
R2.3	120R	ZD2	12V 400mW
R4.5	47R	ZD3	12V 1W
R6	470R	ZD4	5.1V 400mW
R7	100R	ZD5	5.1V 1W
CAPACITO C1,6 C2 C3-C5	ORS 470u 50V electrolytic 2200u 16V electrolytic 1000u 25V electrolytic	Transfe Switch	s pattern ormer PL15-5VA o DPDT toggle flex & plug

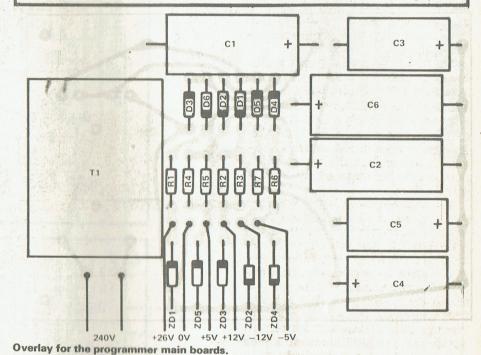

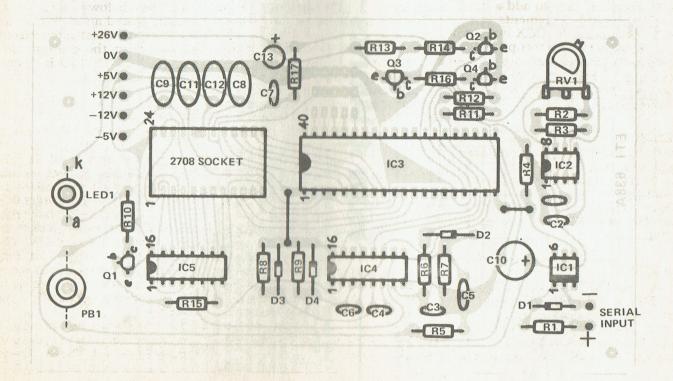

EPROM Programmer

+26V 127 100 2D4 5.1V 400mW 2D3 12V 1W ZD2 12V 400mW ZD1 27V 3 R5 478 R3 120R R7 100R R4 47R R6 470R 3 181 14 470. 1,C5 + C4 - 10000 + C3 +LC2 00 D4 20 Power supply of the 71 240V-15VCT (PL15:5VA) eeeleee programmer. 240V

is connected to the microprocessor's serial port which is configured for the appropriate signal format selected for the programmer (see table 3). The programmer is then reset to initialize the UART and ensure that the address counter starts at address zero. All that remains is for the microprocessor to output the contents of the selected RAM page, byte by byte at the port. As the programming pulse width is approximately 1ms, the whole 1024 bytes should be output at least 100

times. In practice, this should be increased by 25% or so to allow for the effects of component tolerances.

Programmer Design

Use of the UART considerably simplifies the software requirements of the system which will drive the programmer, all that is necessary is a program which will output the required memory contents in order and repeat this for the required number of times.

How it Works-

A fully erased EPROM has every bit set to the "1" state. Programming sets selected bits to "0". To program a 2708 the selected address and corresponding data has to be presented to the EPROM and a 26V pulse applied to the program input pin. To make life more difficult each location has to be selected and programmed in sequence. Also a total time the program input has to be high for each location is 100 ms but the pulse used cannot be less than 100us or longer than 1 ms with about 1 ms recommended. This means that the IC has to be cycled through completely around 100 times for best results!


As we have a computer anyway (otherwise why the need for an EPROM!), we use it to provide the sequencing and timing needed.

The computer is programmed to copy data in its memory (1024 bytes) and sequentially transmit in serial form each byte 125 times. It also pauses for about ¼ second each 1024

The serial information is transferred from the 20 mA loop into a 0-5V signal by the opto coupler, ICI, whose output is fed into the input of the UART IC3. This IC then converts this information into parallel form on pins 5-12 which is presented to the EPROM on its data lines. This IC needs a clock input at 16 times the Baud rate (4800Hz for 300 Baud) and IC2 is used for this.

supplied by IC5 which is a 12 bit-binary counter (we use only the first 10 bits) and this The address lines for the EPROM are is reset to zero when no data is being received. On pin 19 of the UART we have an output which goes high when the serial data has been received and after this has been delayed by about $100 \mu s$ (R6/C3) the output of IC4/1 goes low. This triggers a 1 ms monostable (C4, R8, IC4/3) which drives the transistors Q2-Q4 to provide a 26V pulse to pin 18 of the 2708. At the end of this 1 ms pulse a second mono is triggered (C6, R9, IC4/4), the UART is reset (pin 19 goes low mented. The output (pin 19) of IC3 also charges C5 via D2 when it goes high. This causes the output of IC4/2 to go low allowing regularly corresponding to data being error which may have been caused by a again) and the address counter IC5 is increline). Provided the output of IC3 goes high received at 300 Baud C5 does not have time to there is a pause at the end of a complete cycle the reset line will go high and will correct any IC5 to be toggled (pin 11 of IC5 is the reset discharge and the reset line remains low. If possible glitch.

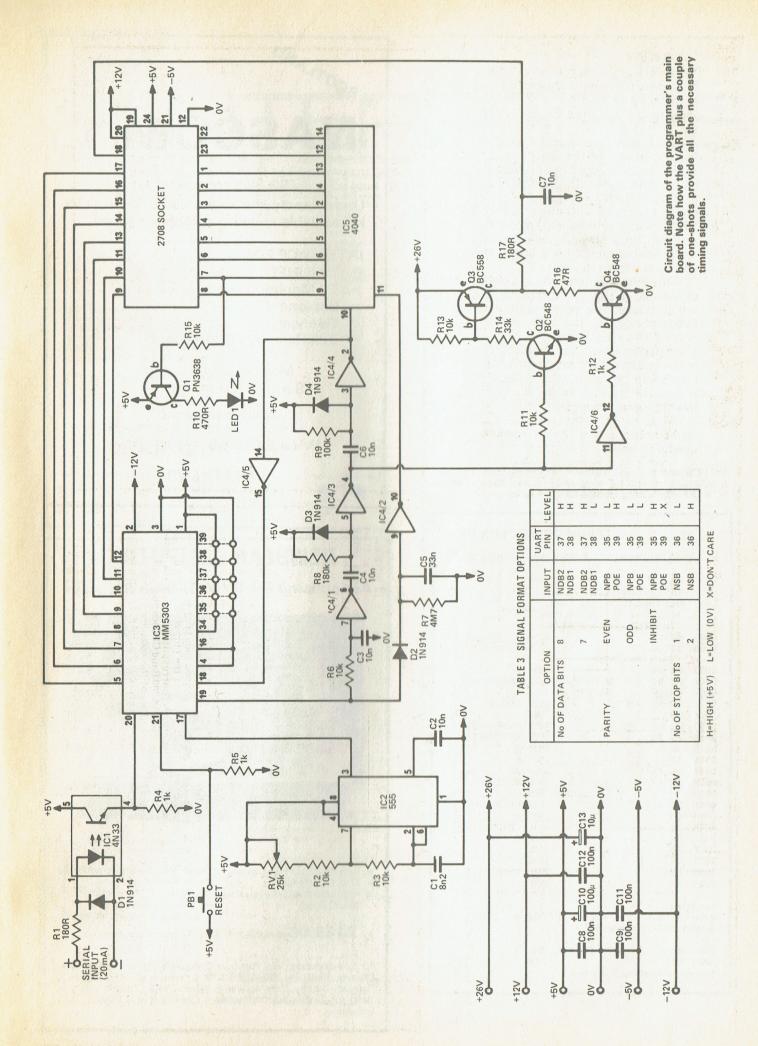of the outputs of IC5 and is turned on and off quickly indicating data is being received.



Construction

We built our prototype into a plastic best with the power supply on one board in the box itself while the logic board was used in place of the

These boards should be assembled according to the overlays provided. Normal handling procedures should be taken with the CMOS ICs and the UART. A good quality socket should be used for the EPROM as it will be used a lot. The pushbutton, LED and power switch are mounted on the logic board and connected from the rear.

With the power switch, due to the closeness of the capacitors on the lower board, the wires should be taken parallel to the PCB and the rear of the switch epoxied over to give protection. The connection between the power supply and logic board can be done with a piece of ribbon cable as the connections follow the same sequence.

We used PC pins for the data input points but a socket could be used if desired.

The PCB patterns for this project can be obtained by sending an SAE to Computing Today, 25-27 Oxford Street, London, WIR IRF. Mark the envelope EPROM foils.

TABLE 1. 6800 EPROM DRIVER FOR D2

6800 EPROM PROGRAMMER DRIVER FOR D2

				TOURANINI	En	יוחע	VEN	run i	12
	OU	TCH		EQU	E3	7A			
	PA	GES1	ART	EQU	04				
	NE.	XTP/	AGE	EQU	80				
		IAS			80				
	; IN	ITIA	LISA	TION OF AC	CIA	1			
0000	86	55				LDA	A	# %0	101001
0002	B7	80	80			STA	A		
	; M.	AINI	PROG	RAM					
0005	C6	7D				LDA	В	125	
0007	CE	00	00	NEWCYCL	E:	LDX	PA	GESTA	RT
000A	A6	00		NEXTBYT	E:	LDA	A,	X	
000C	BD	E3	7A			JSR	OU	TCH	
000F	80					INX*			
0010	8C	04	00			CPX	NE:	XTPAC	E
0013	26	F5				BNE	NE.	XTBY1	E
0015	36					PSH	A		
0016	37					PSH	В		
0017	86	FF				LDA	A	\$FF	
0019	C6	FF				LDA	В	\$FF	
001B	5A			LOOP	:	DEC	В		
001C	26	FD				BNE	LO	OP	
001E	4A					DEC	A		
001F	26	FA				BNE	LO	OP	
0021	33					PUL	В		
0022	32					PUL	A		
0023	5A					DEC	В		
0024	26	E1				BNE	NE	NCYCL	E
0026	3F					SWI			
For Te	st:								
000A	86	XX		NEXTBYT	E:	LDA	A	XX	
output	s AS	CII	charac	ter XX					
or									
000A	4C			NEXTBYT	E:	INC	A		

NOP

IN SCOTLAND

IN SCOTLAND

NASCOM

Z80 Microcomputer kit Undoubtedly the finest value for money kit available anywhere. Fully socketed.

INTERFACE FOR:

TV (UHF) TV Monitor Cassette Teletype 32k Ram expansion board

> May be seen working 9 a.m. - 5 p.m. Mon.-Fri.

> > Callers welcome

Price £197.50 + VAT (8%)

Callers welcome Buy it with Acces

STRATHAND 44 ST. ANDREW'S SQ.

GLASGOW G1 5PL


041-552 6731 Tel. order welcome with Access and Barclaycard

Callers welcome



NEWBEAR COMPUTING

Announcing the SYM-1:-from Synertek

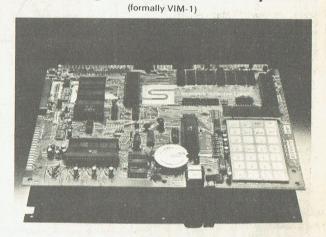

- ★ Fully assembled and tested KI M.I. compatible.
- High speed cassette interface (2400 baud)
- ★ 1K byte storage, expandable on board to 3K byte
- 4K byte ROM Monitor
- * Fully expandable and much much more

£199.00 plus 8% VAT £1.00 postage and packing

For further details. Visit Newbear Computing Store, 2 Gatley Road, Cheadle, Cheshire, 061-491 2290. Or visit, or write to: Newbear Computing Store, 7 Bone Lane, Newbury, Berks. 0635 49223. Send for Catalogues of Hardware Components, Literature and Software.

000B 01

outputs incrementing characters.



From the representatives in Europe ... for America's leading Micro-computer magazines and books, for the hobbyist, educationist and professional alike, we bring you a little light browsing! Reading maketh a full man . . . Francis Bacon (1561-1626)

Tick or indicate quantity ordered.	
From Adam Osborne Associates	Price UK
INTRODUCTION TO MICROCOMPUTERS	
Volume 0: The Beginners Book	£5.95
Volume 1: Basic Concepts	£5.95
Volume 2: Some Real Products (Revised Late 1977)	£11.95
6800 Programming for Logic Design	£5.95
8080 Programming for Logic Design	£5.95
Z80 Programming for Logic Design	£5.95
8080A/8085 Assembly Language Programming	£6.95
6800 Assembler Language Programming Some Common BASIC Programs	£6.95 £5.95
Some Common BASIC Programs	13.93
BUSINESS PROGRAMS IN BASIC	
Payroll With Cost Accounting	£9.95
Accounts Payable & Accounts Receivable	£9.95
General Ledger (Available from late summer 78)	£9.95
From Scelbi Computer Consulting Inc.	
6800 Software Gourmet Guide & Cookbook	£7.95
8080 Software Gourmet Guide & Cookbook	£7.95
8080 Programmers Pocket Guide	£2.25
8080 Hex Code Card	£2.25
8080 Octal Code Card	£2.25
8080 Guide and One 8080 Code Card 8080 Guide and Both Code Cards	£4.20 £6.00
Understanding Microcomputers & Small Computer Syste	
SCELBI 'BYTE' Primer	£9.95
8080 Standard Assembler (In Block Format)	£15.95
8080 Standard Editor (In Book Format)	£9.95
8080 Standard Monitor (In Book Format)	£9,95
From Peoples Computer Company	
Reference Books of Personal & Home Computing	£4.95
What to Do After You Hit Return	£7.00
Dr. Dobbs Journal Volume 1	£10.00
*From Kilobaud/73 Magazine Inc. Hobby Computers Are Here	€3.95
New Hobby Computers	£3,95
New Hobby Computers	20.00
From Dymax Inc.	
Instant BASIC by Jerald R. Brown	£4.95
Your Home Computer by James White My Computer Like Me When I Speak	€4.95
BASIC By Bob Albrecht	£1.65
Games With A Pocket Calculator by	ELIOU
Thiagarajan & Stilovitch	£1,75
Games, Tricks and Puzzles For a Hand	
Calculator by W. Judd	£2.49
*From BYTE Publications Inc.	
Paperbytes:	
Tiny Assembler for 6800 Systems	£5.75
Bar Code Loader for 6800, 8080, Z80 & 6502 Micros	£1.75
Best of Byte Volume 1	€8.95

Francis Bacon (1561-1626)		
Tick or indicate quantity ordered	Price	Price
* From Creative Computing Press	UK	Overseas
Best of Creative Computing Volume 1	£6.95	If Different
Best of Creative Computing Volume 2	£6.95	
BASIC Computer Games	05.50	
(A revised 101 BASIC Games)	£5.50	
The Colossal Computer Cartoon Book	£3.95	
Computer-Rage (A new Board Game)	£6,95	
Artist and Computer	£3.95	
* From Everyone Else	Maria dista	
Magazine storage boxes (hold 12 minimum)	£1.25	
Sybex: Microprocessors from Chips to Systems		
by R. Zacs	£7.95	
Sybex: Microprocessors Interfacing Techniques		
by R. Zacs	£7.95	
Dilithium: Home Computers		
Volume 1: Hardware	£6.50	
Dilithium: Home Computers		
Volume 2: Software	£5.95	
Getting Involved With Your Own Computer	£4.75	
The Z80 Microcomputer Handbook	£7.50	
TV Typewriter Cookbook by Don Lancaster	£7.50	NO 2014 .
TTL Cookbook	£7.95	
CMOS Cookbook	£7.95	
IC Timer Cookbook	£7.50	Maria Control
IC OP—AMP Cookbook	£9.50	
RTL Cookbook	£4.25	
Computer Programs that Work (in BASIC)	£2.55	
* From Basic Software Library		
(from Scientific Research Instruments)		
Vol 1: Business and Personal Booking Programs	£17.50	
Vol 2: Maths and Engineering Programs	£17.50	
Vol 3: Advanced Business Programs	£26.50	
Vol 4: General Purpose Programs	£7.95	
Vol 5: Experimenters Programs (General	L1.33	
Purpose)	£7.95	
Vol 6: General Ledger Program	£32.50	
Vol 7: Professional Programs		
Magazines: Rock Issues	£26.95	
Magazines: Back Issues	£1.75	
Personal Computing Interface Age	£2.25	
Dr. Dobbs Journal	£1.75	
Computer Music Journal	£2.50	
Peoples Computers	£1.75	
*BYTE	£2.25	
Creative Computing	£1.75	
Calculators & Computers	£1.75	
ROM	£1.75	
Kilobaud	£2.25	
73	£2.00	
MAGAZINES: Subscriptions	01000	
Personal Computing (Twelve Issues Yearly)	£16.00	
Interface Age (Twelve Issues Yearly)	£20.00	
Dr. Dobbs Journal (Ten Issues Yearly)	£13.00	
Computer Music Journal (Four Issues Yearly)	£8.50	
Peoples Computers (Six Issues Yearly)	£8.00	
Kilobaud (Twelve Issues Yearly)	£20.00	£21.00
BYTE (Twelve Issues Yearly) via USA	£15.00	
BYTE (Twelve Issues Yearly) via UK	£21.00	
Creative Computing (Six Issues Yearly)	£8.50	
Creative Computing (Twelve Issues Yearly)	£16.00	
Calculators & Computers (Seven Issues Yearly)	£10.00	
73 (Twelve Issues Yearly)	£20.00	
	220.00	

HOW TO ORDER

Please note our prices include postage and packing, but not insurance, if wanted add 12p for every £10 of books ordered. Make cheques, PO's etc pay-

able to

L.P. Enterprises

CREDIT CARDS accepted.

BARCLAYCARD VISA/ACCESS

DINERS CLUB/AMERICAN EXPRESS

Phone: 01-553 1001 for Credit Card orders (24 hour service).

Due to fluctuations of the dollar, prices are subject to change

Send to address above for the attn. of David, Dept. ETI/12 Indicate Payment Method:	All Orders must be Prepaid Total Enclosed £
My cheque, P.O., I.M.O. is enclosed in Sterling on U.K. Bank	
Charge to Barclaycard/Visa/Access/Diners/American Express	
Credit Card No	and the American
Name	
Address,	
	POSTCODE
Signature	v

All publications are published in U.S.A. and shipped air-freight by L.P. Enterprises. In unusual cases, processing may exceed 30 days
*BYTE subscriptions are processed IN USA and are air-freighted & posted from Amsterdam and will take 3 months to start.

U.K. Subscriptions start within three weeks

TRADE ENQUIRIES WELCOME

STUDENTS & TEACHERS WITH YOUR ORDER, SEND PROOF OF YOUR STATUS AND RECEIVE 5% OF YOUR PRESENT ORDER AS A CREDIT CERTIFICATE YOU USE ON YOUR NEXT ORDER. CHRISTMAS SPECIAL OF 5% OF ORDERS MAILED BEFORE DECEM THE FIRST MEMORY SPECIAL 2102-2 8/995 650ns 8/1095 2102-4 450 ns 8/7900 2114D 450 ns PRESCALER - 250 MHZ complete \$2395 PRESCALER - 650 MHZ complete \$4995 11C90 - PRESCALER CHIP 650 mc SOLID STATE RELAY • 400 V at 3 AMPS • TTL COMPATIBLE • MICRO REED ACTUATED TO MINIMIZE CHANCES OF AC POWER SPILLOVER INTO LOGIC CIRCUITS CHEAPER BY THE 100

LEDS

LEDS-

1	ANY OF T	HESE I.C.'s.	
	FECTIVE ON 25, 1978.	ALL	
YOU	WON'T F	ORGET	
700	64/7100	128/13500	
100	64/7800	128/14500	
4900	32/27400	64/49900	
T		A SA	

32/3

32/4

16/1

\$1995

100/8.95

100/13.95

FREE SOCKETS

WITH PURCHASE OF

32/27400	64/499	00
	AUTO TO	dian.
OPTO		
ISOL	ATOR	S
1. MCT2	\$.79
2. MOC10	000 \$.89
3. 4N-26	\$.95
4. CL142	2	
	ното мор	
(USE AS VO		
RESISTOR-		
40 OHM-N		
RATIO-OR		
HIGH VO	LTAGE	OPTO
ISOLATOR)		

REFLECTIVE

PHOTO COUPLERS

TIL-139 LED INTO PHOTO

ROC100 INCANDESCENT

OHM

TRANSISTOR

RESISTANCE

20

INTO CDS CELL-

MEG

\$149

\$295

OFF

1850

\$195

3880	22.50
3881	12.50
3883	49.00
3884	73.00
	SYSTEM
6800	16.95
6810	7.20
6820	7.95
6821	7.20 7.95 8.50
6850	8.95
6852	11.95 9.95
6860	9.95
6852 6860 6862	13.75
6500	SYSTEM
6502	14.95
6520	12.75
0522	12.50
6530	17.50

Z-80 SYSTEM

8080 SYSTEM

9.45

8080A

8212 8214

8228 8238 8251

8253

CPU's cont.

RAM

19.95

4.95 4.95 11.95 3.95 3.95 3.95

13.50 10.95 6.25 18.50

8035

7489

3101

2102-2 2102L1

82S11 5101L-3 2107 TMS4060 UPD411 4200A

200 ns 450 ns 650 ns

200 ns

PROG. LOGIC ARRA

SHIFT REGISTERS

82S101

C14024 MM1403AH MM5006AH MM5060

MM5312

MM5313

MM5314

MM5316 MM5375 TMS3834 CT7001

MM5725 MM5736

DS0026 DS3608

DM8093 DM8094

DM8131

DM8202

DM8233

DM8234

DM8241

DM8242

DM8267

DM8271

DM8544

DM8831 DM8833 DM8835 DM8836 DM8837

14273

CALCULATOR CHIE

INTERFACE CHIPS

1	8 95	PROM	5
2	11.05	8223	2.95
0 2 0 2	8.95 11.95 9.95	82S23	3.75
,	13.75	82S126	5.95
4	13./5	82S129	6 05
00	CHOTESA	82S131	6.95 7.25 6.95 5.95 11.95
00	SYSTEM	6306-1	6.05
2	14.95 12.75 12.50 17.50	93427	0.93
0	12.75	9342/	0.95
2	12.50	D3604	11.95
)	17.50		
		1702A	4.95
00	SYSTEM	2708	4.95 12.95 46.95
0	66.00	2716-5V	46.95
1	23.75		
2	66.00 23.75 19.50 54.00 54.00	CHARACTER GE	MERATORS
0	54 00	TO STATE OF THE PARTY OF THE PA	PATE AND DESCRIPTION OF
ĭ	54.00	2513 UC	7.95
	34.00	2513 LC	7.95
00	SYSTEM	2516	7.95
UU	3131EM	5240	7.95
	24.00	2513 LC 2516 5240 MM6571A	9.95
1	19.50		
4	20.25	KEYBOARD I	
1	13.50	AY5-2376	14.95
2	13.75		
6	11.75	UART	
7	11.76	AY5-1012	
1	24.00 19.50 20.25 13.50 13.75 11.75 11.76 20.00	AY5-1013	
		TR-1602	9.95
C	PU's	TMS6011	8.95
0	10 05	The state of the s	VI TAMBOUR OF

FIFO's

ALL SHARE	
	CARA MOTUER ROADS & CLAVA COR
IYS	S-100 MOTHER BUARD — 8 Slot Kit 69.00
95	S-100 32K STATIC MEMORY BOARD
95	ALL BURNED IN 950 us 599.00
s	AND 1ESTED 450 ns 735.00
2	ultra low power 200 ns 8/5.00
95	S-100 EDGE CARD CONNECTORS 3.50
95	MAXI KEYBUARD — 53 Keys 19.95
95	MAXI KEYBOARD — 74 Keys 33.95
95	KEYPAD — 16 key x-y matrixed 1.95
4/1	S-100 MOTHER BOARD — 8 Slot Kit
95	2 level 100/3.95 4 level 100/4.95
95	WIRE WRAP SOCKET PIN 100/7.95
95	TAPE READER — 12 level — includes both
95	IR sources and pickups 29.00
95	MAKE YOUR OWN PAPER TAPE READER
50	1/10" SPACED PHOTO TRANSISTORS 10/9.50
95	REED RELAY — TTL compatible 1.89
95	SOLID STATE RELAY — micro reed actuated
50	for total isolation 3.95
	CRYSTAL FILTERS — 455 Kc miniature
PS	single section 1.95 dual section 2.95
95	
95	MARK YOUR OWN PAPER TAPE RADER 10/9 50
95	YSI BEAD — 1% 5000 OHM 2.95
95	GLASS BEAD — 1% 15000 OHM 2.95
95	GLASS BEAD — 1% 200 OHM 2.95
1000	CYLINDRICAL — .01%
S	POWER THERMISTOR — positive temperature
25	coefficient 20-2500 OHM 2.95
85	D/A CONVERTED NESONS (9 NA 7 05
95	D/A CONVERTER — NESOUS (8 BIL) 7.33
95	PHOTO DIODE super fact 0 5 cc 2 05
95	IP DETECTOR super capatitus 4.05
95	IN DETECTOR — Super Sensitive 4.55
95	D/A CONVERTER
95	READ OUTS — MULTI DIGIT LCD-3-1/2 dig. 4"-4.95 3-1/2 dig. 3" 1.95 LED .17"-3 dig. 1.25 — 6 dig. 3.95 — 8 dig. 4.95
25	IED 17" 3 dig 1 25 — 6 dig 3 95 — 8 dig 4 95
45	
10	PHOTO DEVICES—DIODES. XSTR's, DARLINGTONS 2N5771 · 1.25
10	2N5771 . 1 25 FPT100A . 79 MD1 .1 95
45	H.38 - 3.25 MRD.250 - 1.95 LASCR 1.95
45	1130 0.23 1110 230 1.33 2.300 1.33
	HICH VOLTACE TRANSISTORS
90	2001259 100W 1400V 54 TO 2 7.05
90	23C1336 100W-1400V-3A 10-3 7.93
35	DUTO3D 110W 500V-10A 10-3 5.95
35	W905 100W- 500V-5A Plastic 4.95
35	302-4 20W- 500V-1A Plastic 2.25
30	338-7 20W- 350V-1A Plastic 1.50
95	
60	HIGH VOLTAGE DIODES
60	HIGH VOLTAGE TRANSISTORS 2SC1358 100W-1400V-5A T0-3 7.95 BUY69B 110W-800V-10A T0-3 5.95 W905 100W-500V-5A Plastic 4.95 3362-4 20W-500V-1A Plastic 2.25 338-7 20W-350V-1A Plastic 1.50 HIGH VOLTAGE DIODES UNMARKED 1500V at 1 AMP 10/1.99 EG 250 2500V at 35 AMP 95 HV60EL 6000V at 25 ma 1.95 SUBMINIATURE 20,000V at 100 ma 2.95
75	EG 250 2500V at .35 AMP .95
45	HV60EL 6000V at 25 ma 1.95
60	SUBMINIATURE 20,000V at 100 ma 2.95
10	
95	CARBIDE DRILL BITS AND ROUTER BITS
95	for P.C. board work — MIXED SIZES
95	OUR MIX — DRILLS 10/12.95 100/95.00
	CARBIDE DRILL BITS AND ROUTER BITS for P.C. board work — MIXED SIZES OUR MIX — DRILLS 10/12.95 100/195.00 OUR MIX — ROUTERS 10/15.95 100/125.00

SERVICE AND

MODIFICATION

AUDIO POWER AMPS

(HP AXIAL-RED)

LEDS: (JUMBO-RED) 100/13-95 LEDS: (DUAL COLOR) 100/59-00 1N4001- (50V-1 AMP) 100/4-95 1N4148- (SWITCHING DIODE) 100/-3-95 2N4303- (N-JFET) 100/21-95 2N3392- (PRIME-NPN LOW NOISE) 100/-9-95

(MINI-RED)

(IUMBO-RED)

SINGLE TDA-2020-20 Watt \$11020H -20 Watt \$11130H -30 Watt	\$9.95 \$10.50 \$12.50	STEREO STK433-5 Watts per channel \$6.95 STK435-7 Watts per channel \$9.95 STK437-10 Watts per channel \$11.95 STK439-15 Watts per channel \$13.95
STK-50 -50 Watt	\$18.95	STK441-20 Watts per channel \$16.95

D BE FIRST TO TURN YOUR TRS-80 INTO SUPER MACHINE

1. Keyboard and Video Mod

RADIO SHACK

ADD RAM FOR LOWER CASE CHARACTERS AND CLEAN UP HORIZONTAL SMEAR (SEND YOUR TRS-80 MICROCOMPUTER ONLY) PARTS AND LABOR \$5900

4. Clock Mod

INCREASE YOUR PROCESSING SPEED BY 30%. WITH THIS OPTION YOU CAN SWITCH-SELECT BETWEEN THE FASTER 2.66 MHZ CLOCK RATE AND 1.77 MHZ.

INSTALLATION, PARTS AND LABOR \$4900

ALL WORK GUARANTEED UNCONDITIONALLY FOR 1 YEAR

SPECIALS!! DO MORE THAN ONE MOD

MODS 1, 2, 3, 4 AND 5 \$44900 MODS 1 AND 2 \$23400 MODS 2 AND 3 \$24300 16K MEMORY, PARTS AND INSTALLATION DATA \$15900

2. Install 16K Memory

JUST SEND US YOUR TRS-80 MICROCOMPUTER AND WE DO THE REST.

16K OF MEMORY AND LABOR \$18900

5. Serial Printer Interface Mod

OPERATE CRYSTAL CONTROLLED TTY WITH LEVEL 1 OR 2. WE INSTALL SWITCH SELECTABLE BAUD RATES OF 75, 110, 137.5, 150, 300, 600, 1200, 2400, 4800, 9600 OR EXTERNAL. EIA RS232 AND CURRENT LOOP OUTPUT. PARTS AND LABOR \$11900

SEND TRS-80 KEYBOARD ONLY!!

FROM ENGLAND ADD \$30.00 FOR AIR, \$9.50 SURFACE MAIL FROM JAPAN ADD \$35.00 FOR AIR, \$8.50 SURFACE MAIL

3. Level 2 plus 1 Mod

WE INSTALL YOUR LEVEL 2 SO YOU KEEP LEVEL 1 AND CAN USE IT BY JUST FLIPPING A SWITCH. (SEND LEVEL 2 WITH YOUR TRS-80) \$6900

6. Mini Floppy Mod

YOU PROVIDE EXPANSION INTERFACE AND WE'LL INSTALL A PERTEC F D 200 MINI FLOPPY.

· PARTS AND LABOR (PERTEC F D 200 MINI FLOPPY INCLUDED) FOR ONLY \$42500

REPAIR-WE WILL REPAIR ANY ORIGINAL TRS-80 MICROCOMPUTER OR ONE OF OUR MODIFICATIONS.

ALL PARTS AND LABOR \$6900

NOTE: THIS IS AN INDEPENDENT SERVICE EFFORT NOT AFFILIATED WITH RADIO SHACK® OR TANDY CORPORATION.

TERMS FOR TRS-80 WORK: WE ACCEPT ONLY TRS-80 MICROCOMPUTERS! SHIP YOUR TRS-80 MICROCOMPUTER TO US, AND SUITABLY PACKAGED AND WE WILL RETURN SAME FREIGHT COLLECT. ALL FACTORY SEALS MUST BE INTACT. ANY UNIT WHOSE SEALS HAVE BEEN TAMPERED WITH WILL BE SHIPPED BACK IMMEDIATELY. MODS 1, 2, 4 AND 5 SEND TRS-80 MICROCOMPUTER ONLY. MOD 3 SEND YOUR TRS-80 MICROCOMPUTER AND LEVEL 2. MOD 6 SEND TRS-80 AND EXPANSION INTERFACE. NORMAL TURN AROUND TIME IS UNDER 10 DAYS

1110 E. GARVEY AVE. W. COVINA. CA 91790 (213) 967-3846

• FREE UPS DELIVERY ON
U.S. ORDERS ONLY—OR BY
SURFACE MAIL IF SPECIFIED.

 MONEY BACK GUARANTEE
 (MOS & LED DEVICES EXCLUDED)
 UNDER 8 HOUR PROCESSING MONEY ORDERS & CASHIER'S

• SORRY! NO COD'S, PO'S OR CREDIT CARDS • CALIF. RES. ADD 6% SALES TAX

SALES TAX

CANADA, PUERTO RICO

& U.S. POSSESSIONS
ADD U.S. \$3.50. ALL
OTHERS ADD U.S. \$7.00.

U.S. FUNDS ONLY.

LOS ANGELES (213) 967-4611

LMN ELECTRONICS 1042 E. GARVEY AVE. WEST COVINA. CA

DROP INTO ONE OF OUR LOCATIONS

PORTLAND (503) 646-4044

WIZARD OF PARTS 8225 S.W. CIRRUS DR. BEAVERTON, OREGON

(303) 573-5214

ELECTRONIC LOLLIPOP 5643 N. BROADWAY, DENVER (1-25 & 58th AVE.)

ALL ITEMS SUBJECT TO PRIOR SALE

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

Softspot

The start of a regular software section in Computing Today this month. To start the ball rolling we present a game, designed to run on the TRITON, written by Don Scales. This section will not be restricted to BASIC programs however we want to publish machine code routines, even programming hints.

Send any software you have to Computing Today, 25-27 Oxford Street, London, WIR IRF.

MISSILE (1K)

Missile is a game which utilizes the graphics and memory mapping features available to the TRITON.

The object of the game is to shoot down each enemy aircraft before it gets past your defences (across the screen). To do this you command three missile sites.

Unfortunately, your radar station has been knocked out and the aircraft can come in at any height between 1 and 16 miles high.

The missile stations are sited at 16, 32 and 48 miles from the coast (left edge of the screen). Both the aircraft at 8 miles high, station 1 must fire with a delay of 8 seconds.

There are 10 aircraft coming in and before each, you must set the missile fuses by specifying the time delay before ignition.

Good Luck.

- 10 N = 0
- 20 FOR J = 1 TO 10
- 30 @ (2) = 976, @ (5) = 992, @ (8) = 1008
- 40 a (3) = 976, a (6) = 992, a (9) = 1008
- 50 PRINT 'MISSILE'
- 60 INPUT '1ST' @(1), '2ND' @(4), '3RD' @(7)
- 70 VDU 0, 12
- 80 FOR I = 1 TO 150; NEXT I
- 90 Y=(RDN (16) 1) *61, Z=1 100 FOR X=1 TO 64
- 110 VDU 2, 32
- 120 W = Y + X
- 130 VDU W, 62
- 140 Z=W
- 150 FOR I=1 TO 7 STEP 3
- 160 IF X < @ (I) GOTO 250
- 170 VDU @ (1+2), 32
- 180 IF @ (I+1) < 1 GOTO 250
- 190 VDU @ (I+1), 94
- 200 @(I+2) = @(I+1)
- 210 @ (I+1) = @ (I+1) -64
- 220 IF @(I+2) = W GOTO 400
- 250 NEXT I
- 300 NEXT X
- 310 GOTO 500
- 400 VDU W, 42
- 410 N = N + 1
- 500 NEXT J
- 510 PRINT 'HITS', N

COMPUTING TODAY — DECEMBER 1978

The exciting new **Triton computer from**

ectronics today



The first British-designed home computer kit with basic IN ROM and graphics. The single-board design makes the computer easy to construct and when complete, a very compact and powerful tool for home, educational and industrial use

ADD A STANDARD domestic TV set and a cassette recorder to the TRITON and you have a complete home computing system that is equal to, indeed in some areas superior to, many of the commercial ready built systems now on the market

The TRITON has been designed on a single board, which means that construction should not pose any problems providing an adequate standard of soldering is maintained throughout. The case, designed specifically for the TRITON, means that the finished unit can safely and attractively be housed. In use, with the TV set on top of the case, the TRITON will be easy and convenient to operate.

The TRITON is based on the 8080 MPU, a device which has proven itself over a number of years. This MPU has a vast amount of software available for it and the TRITON'S 1K monitor system allows for easy entry and subsequent modification of such material.

The 2K TINY BASIC that is also resident in the TRITON, allows this popular, easy to learn, language to be used in conjunction with the TRITON's versatile graphic character set and unique VDU function to develop everything from games to education programmes quickly and easily

The TRITON has space for 3K of user RAM on board but the machine has been designed in order to make expansion a simple matter

Complete kit available immediately for only





+ 8% VAT POST PAID

All components can be bought separately. Send s.a.e. 121/2p for full parts and price list. Triton manual is available for £5 (free with kit)



All mail to: Henry's Radio 404 Edgware Rd. London W2 PHONE (01)723 1008

INTERESTED IN HOME

Nascom Microcomputers

Start now and don't get left behind THE NASCOM 1 is here

Ex-stock with full technical services

BLANK C12 Racal Quality CASSETTES £4.00 for 10

Plus the opportunity to join the fastest moving club of personal computer users enabling you to get the most our of your computer. You can OBTAIN and EXCHANGE programs and other software - many now available.

The Powerful Z80 Microprocessor Professional Keyboard 1 Kbyte Monitor in EPROM 2 Kbyte RAM (expandable) Audio Cassette interface Plugs into your domestic TV

Easy construction from straightforward instructions no drilling or special tools Just neat soldering required.

Only £197.50 + 8% VAT (includes p & p + insurance)

Manuals seperately Z80 programming Manual 6.90 IMPROVED TV Z80 Technical Manual PIO Technical Manual

3.50 MONITOR QUALITY 3.40 MODULATOR 3.40 Power supply suitable for

(All prices add 8% VAT) NASCOM 19.90
NASCOM EXPANSION Our customers will be informed within 24 NASCOM hours when we receive Nascom expansion boards

Introducing the personal computer you've waited for. THE EXIDY SORCERER. SEE INSIDE BACK COVER OF THIS MAGAZINE

VIDEO GAMES & Componen

5.90

UHF Vision modulator Standard channel 36 3.10 VHF Vision modulator channel 3 2.90 Sound modulator compatible with above AY-3-8500 6 Games 4.90 PCB 1.90

SPECIAL FOR CHRISTMAS

STOCK CLEARANCE **READY TO GO 4 EXCITING NEW GAMES** £27.90 £19.90 complete with power supply

AY-3-8603 Road Race 5.90

AY-3-8610 10 Games

8500 6 game colour basic kit reduced from £16.90 to £7.90 ETI Tank colour add on -£5.90 8610 10 game chip + PCB - £6.50

JOYSTICKS - £1.90 each Dual 200K lin



PCB 1.90

KEY BOARD

Brand new professional ASCII keyboards (USA) Full technical details

Only £49.90 +8% VAT

included.

Ready built, tested and guaranteed.



LABLE NOW

\$100 BUS Shugart mini floppy drives £290 each

Floppy drive controller direct from USA

£250 each



2.50

Complete with hardwear which neatly packs into a stylish plastic Joy Stick Case plugging directly into your Nascom PIO Port with no extras. FULL DOCUMENTATION SUPPLIED.

Each Joy Stick is supplied with a test routine that allows you to draw pictures on your VDU step routines to write your own games, plus one free game on cassette.

1 JOY STICK £14.90 1 PAIR JOYSTICKS £28.90
The Nascomsoftware users book is being compiled; if you would like your program included, please send with a SAE and in return you will get a copy of the book when it is completed.

B Bug Monitor for Nascom users- Well worth the money £23.40 Send SAE for details.

8 pin 50p 14, 16, or 18 pin £1.00 PRICES FOR PACKS OF 10

22, 24, 28, or 40 pin £1.50

COMPUTER COMPONENTS

A selection of our Computer components

CPU AND SUPPORT DEVICES MEMORIES **Z80** 14.90 cpu 19.90 cpu Z80 780 CTC 9.90 8080A 5.90 8 Bit I/O Port 1.90 8212 Priority Interrupt Control Bi-Directional Bus Driver 4.90 8214 Clock Generator & Driver (2MHz) Clock Generator & Driver (4MHz) 8224 2.50 7.90 Inverting Bi-Directional Bus Driver System Controller & Bus Driver System Controller & Bus Driver 8226 8228 8238 3.90 5.90 Programmable Communication Int. Programmable Interval Timer 8251 7.90 8255 Programmable Peripheral Int. 10.90 8257 8259 Prog. Direct Mem. Access Cont Programmable Interrupt Cont. 14.90 17.90 11.90 4.95 6800 128 x 8 Static Ram (450ns) 128 x 8 Static Ram (250ns) Peripheral Interface Adaptor 68B10P 6.00 6820P 6821P Peripheral Interface Adaptor 7.50 Priority Interrupt Controller 512 x 8 Bit Erasable Prom. 500 6828P 16.95 Asynchronous Comm. Adaptor Synchronous Serial Data Adaptor 6850P 9.75 6860P 10.00 0-600 RPS Modem 6862P 2400 RPS Modulator 14.50 Clock 28.00

1	White the state of	
	8×21L02 1K	7.50
	21L02 1K	1.00
	2101 1K	2.95
١	2111 1K	3.95
ı	2112 1K	2.95
١	2114 4K	6.90
1	4027	2.10
ı	4116 16K	11.90
١	8×4116 16K	90.00
١	2708 1K	7.50
١	2700 (NIACRIIC)	0.00

OTHER USEFUL DEVICES

2716

6576	char gen	8.90
6402	UART	9.90
1771	Floppy disk	
	controller	24.90

(5V, INTEL) 29.00

Full selection of US and British Magazines and books for the Computer

Prices always changing (usually downwards) Phone with your requirements



All prices include VAT except where shown. Orders over £5 post and packing free otherwise add 20p. Please make cheques and postal orders payable to COMP, or phone your order quoting BARCLAYCARD or ACCESS number.

6875P

Clock

MPU Bidir. Bus Ext.





COMPUTER COMPONENTS 14 STATION ROAD · NEW BARNET · HERTFORDSHIRE · Tel:-01-441 2922 (Sales) 01-449 6596 CLOSE TO NEW BARNET BR STATION - MOORGATE LINE

OPEN-10am to 7pm-Monday to Saturday

8.75